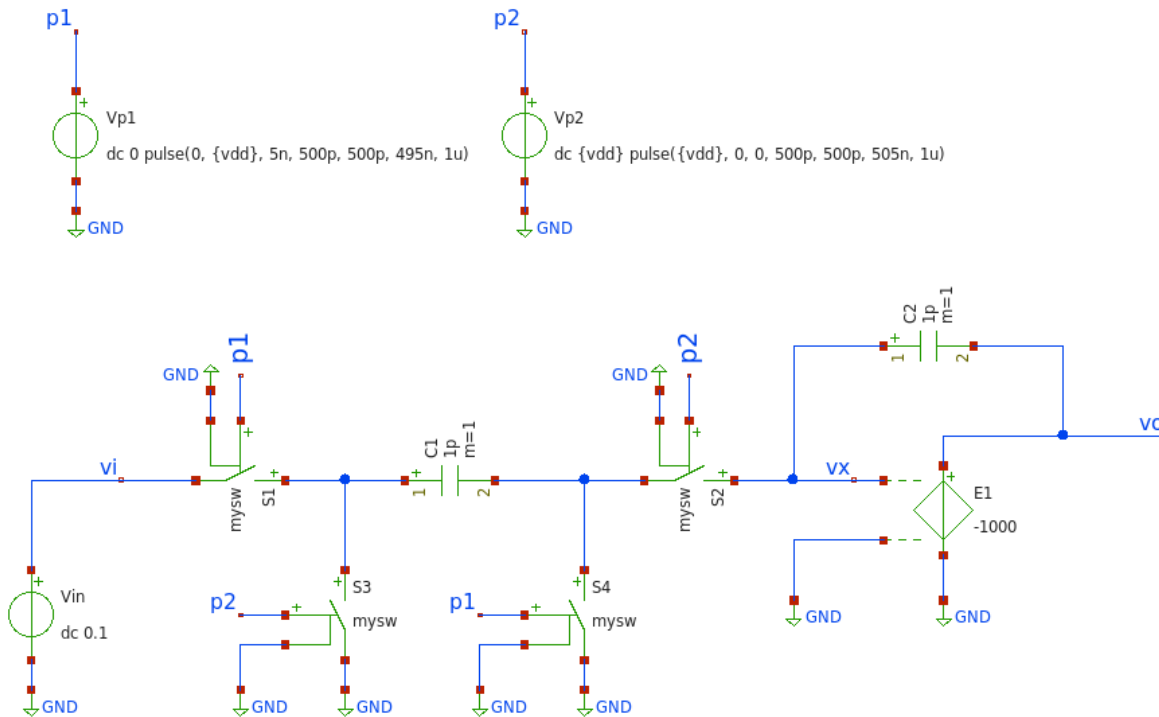


Amplifier

Boris Murmann

bmurmann@hawaii.edu

Switched-Capacitor Integrator



NGSPICE

```
.param temp=27 vdd=1.2
.model mysw SW vt={vdd/2} ron=10k roff=10gig
.control
save all
tran 1n 3u
plot vo
write tb_ideal_integ.raw
.endc
```

MODEL

```
.lib $::SG13G2_MODELS/cornerMOSlv.lib mos_tt
.lib $::SG13G2_MODELS/cornerRES.lib res_typ
```



Boris Murmann


/foss/designs/tb_ideal_integ.sch

2024-01-12 06:00:17


Nonidealities

- Many nonidealities to worry about, especially for the amplifier
- Offset
- Finite gain
- Noise (more later)
- ...



Non-overlapping two-phase clocks

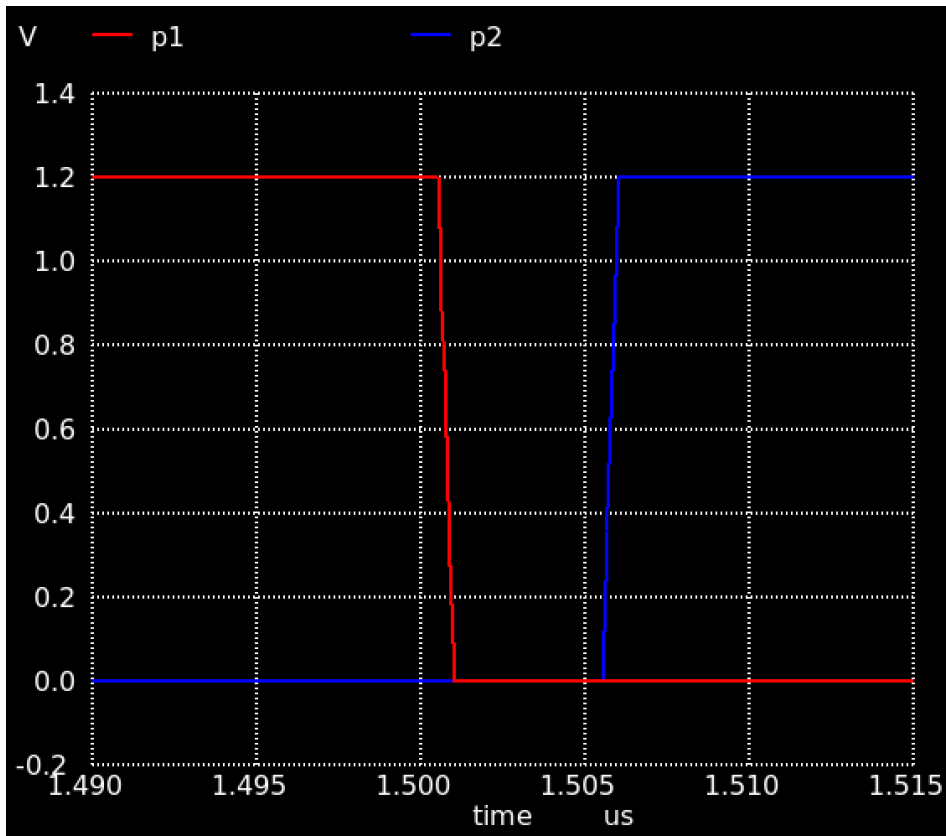

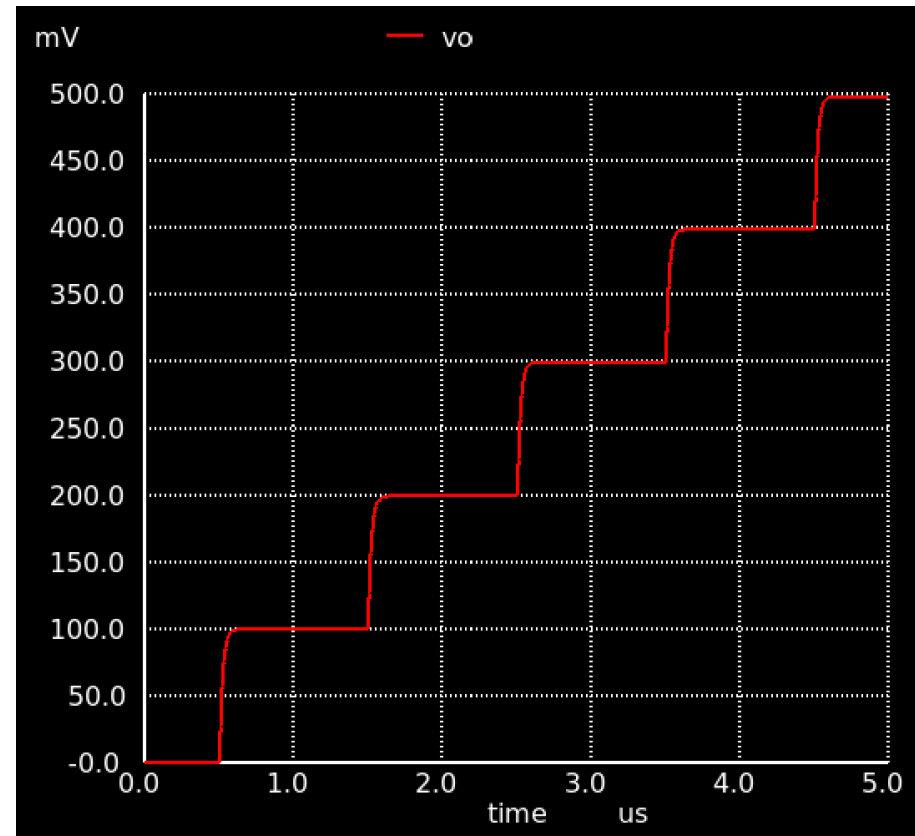
Integrator output
(Amplifier gain = 1000)



Integrator output
(Amplifier gain = 20)

 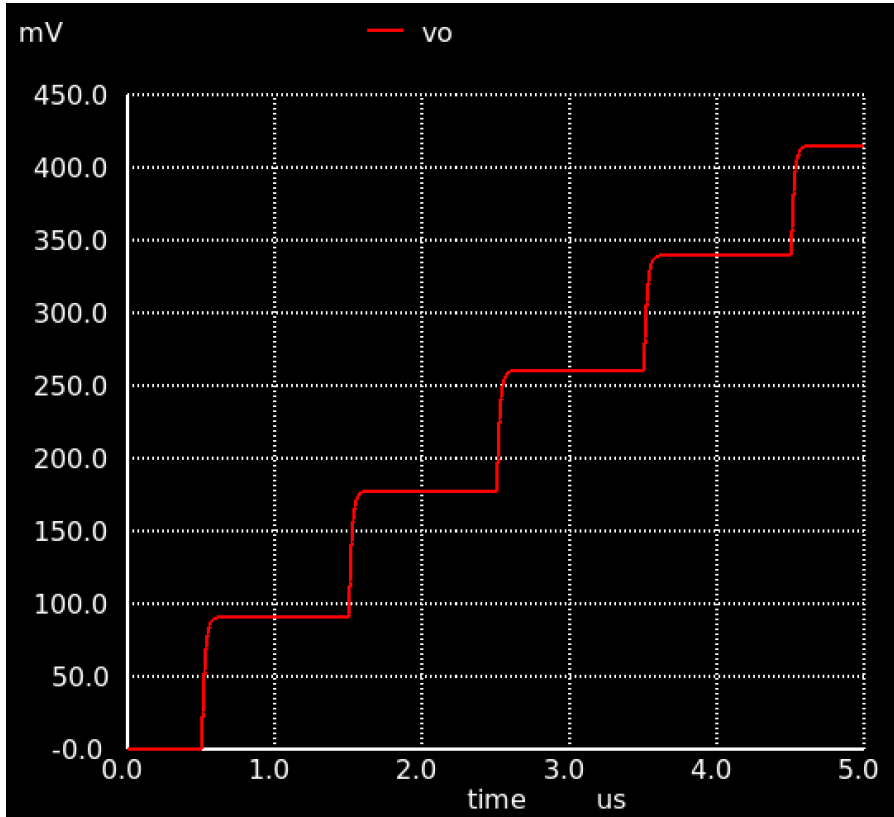


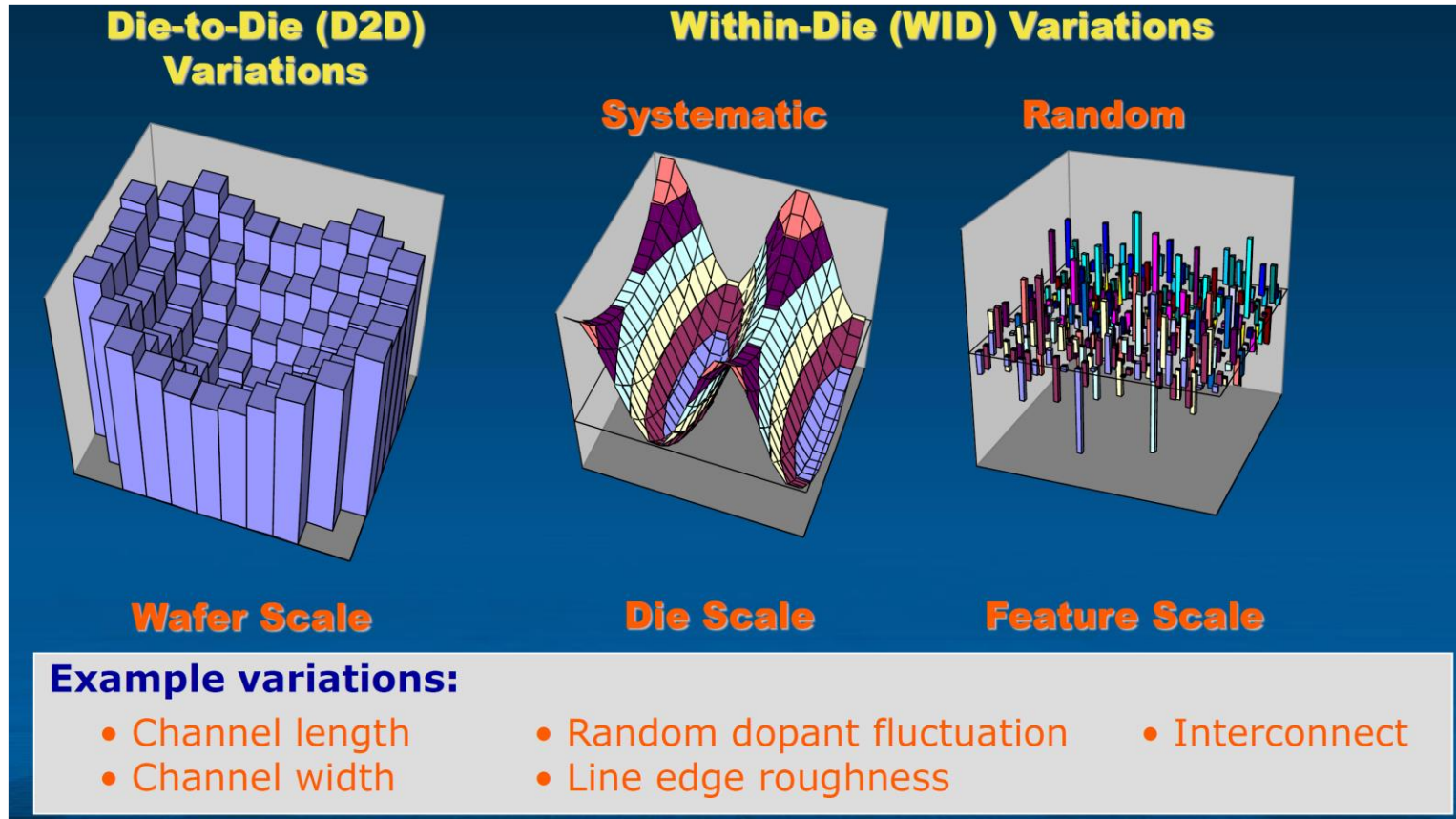
Parameter Variations in Integrated Circuits





[Jim Tschanz, Intel]

Device-to-Device Mismatch

  - Differences between nominally identical devices on the same chip





$$\Delta C = C_1 - C_2$$

  


$$\Delta R = R_1 - R_2$$

$$\Delta V_t = V_{t1} - V_{t2}$$

  

$$\Delta \beta = \left(\mu C_{ox} \frac{W}{L} \right)_1 - \left(\mu C_{ox} \frac{W}{L} \right)_2$$

Equivalent
input offset
voltage

 

Statistical Model


- Experiments have shown that mismatch for closely spaced, properly laid out devices (no systematic errors) is random and Gaussian
- The standard deviation of the parameter mismatch between two devices can be (approximately) modeled using Pelgrom's formula

$$\sigma_{\Delta P} = \frac{A_P}{\sqrt{WL}}$$

- A_P is the Pelgrom matching coefficient
- WL is the device area

| Parameter | Value for 0.18 μm CMOS |
|----------------------------------|-----------------------------------|
| A_{V_t} (MOSFET) | 5 mV- μm |
| $A_{\Delta\beta/\beta}$ (MOSFET) | 1 %- μm |
| $A_{\Delta C/C}$ (MIM capacitor) | 1 %- μm |
| $A_{\Delta R/R}$ (Poly resistor) | 3 %- μm |

Example: SC Gain Stage with Offset

 


$$\left. \begin{array}{l} n: \quad Q_x = 0 \\ n+1/2: \quad Q_x = -V_{os}C_s + [V_{out} - V_{os}]C_f \end{array} \right\} V_{out} = V_{os} \left(1 + \frac{C_s}{C_f} \right)$$

- Offset propagates to output

Correlated Double Sampling (CDS)

- Aims to suppress the offset error by separating it from the signal in the time domain
- There also exists a “chopping” technique that separates the two in the frequency domain
- Basic idea of CDS
 - Subtract two samples, one of which contains the error while the second sample contains the signal + error
 - If the error is strongly correlated between the two samples (error is DC or low frequency) it is cancelled or highly attenuated by the subtraction

SC Gain Stage with CDS


 


ϕ_1 : Autozero phase

ϕ_2 : Amplification phase

Output sampled
at the end of ϕ_2



Autozero Phase

  

$$Q_x = -V_{os}C_s - V_{os}C_f$$

(assuming infinite amplifier gain)

Amplification Phase

  

$$Q_x = -V_{os}C_s + [V_{out} - V_{os}]C_f$$

$$-V_{os}C_s - V_{os}C_f = -V_{os}C_s + [V_{out} - V_{os}]C_f \quad V_{out} = 0$$

Verdict on CDS

- CDS works well for suppressing the offset error and it is widely used
- Unfortunately, it does not help us with errors due to finite amplifier gain
 - The error due to finite gain is proportional to the signal, but CDS measures the error without the signal being present...
- There exists a variety of clever ideas to reduce the gain error
 - Sometimes leading to the effective “squaring” of the amplifier gain
 - K. Nagaraj, T. Viswanathan, K. Singhal and J. Vlach, "Switched-capacitor circuits with reduced sensitivity to amplifier gain," in IEEE Transactions on Circuits and Systems, vol. 34, no. 5, pp. 571-574, May 1987. <https://ieeexplore.ieee.org/document/1086170>

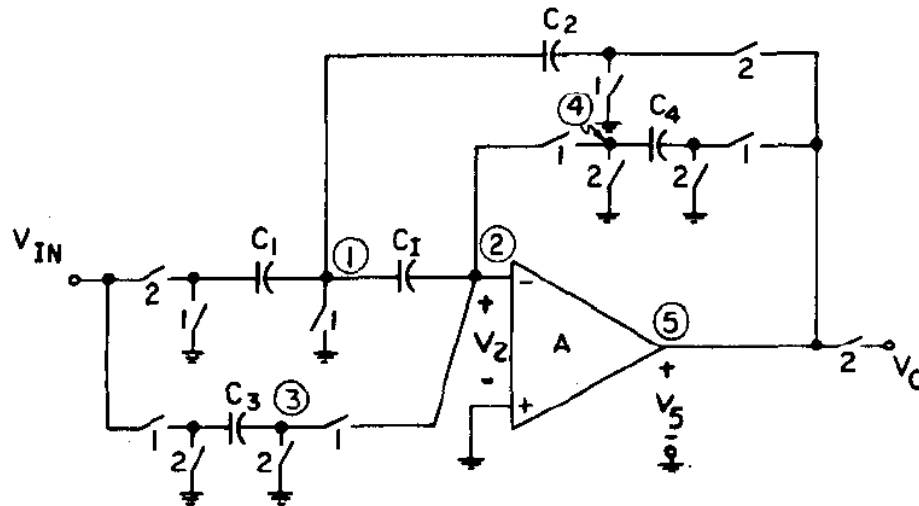


Fig. 1. Circuit schematic of the amplifier/attenuator incorporating the proposed technique.

$$V_0(n) = -\frac{C_1}{C_2} V_{IN}(n) - \epsilon \quad \epsilon = \frac{1}{A^2} \left[1 + \frac{C_1}{C_2} \right] \left[\left(1 + \frac{C_1}{C_2} + \frac{C_I}{C_2} \right) V_0(n) - \frac{C_I}{C_2} V_0(n-1) \right]$$

- Great improvement, but need to process input sample in both half cycles
- Often not practical. Can we do something simpler?

Nagaraj, K., Singhal, K., Viswanathan, T.R., & Vlach, J., "Reduction of finite-gain effect in switched-capacitor filters," Electronics Letters, 21, 644-645, 1985.
<https://designers-guide.org/forum/Attachments/04250650.pdf>

Introduction: One of the important factors limiting the performance of MOS switched-capacitor (SC) filters is the finite gain of amplifiers. It has been shown that in SC filters the effect of finite gain is more serious than that of finite bandwidth.¹ In this letter we propose a simple technique to significantly reduce the finite-gain effect. It is based on the fact that in a vast majority of practical SC filters the sampling frequency is made much higher than the signal frequencies of interest in order to make the required continuous-time anti-aliasing and reconstruction filters easily realisable on silicon (an extensive survey of the literature has revealed that a ratio of at least 20:1 is maintained in most cases). Thus there would be considerable correlation between successive signal samples. This is exploited here to reduce the finite-gain effect.

