
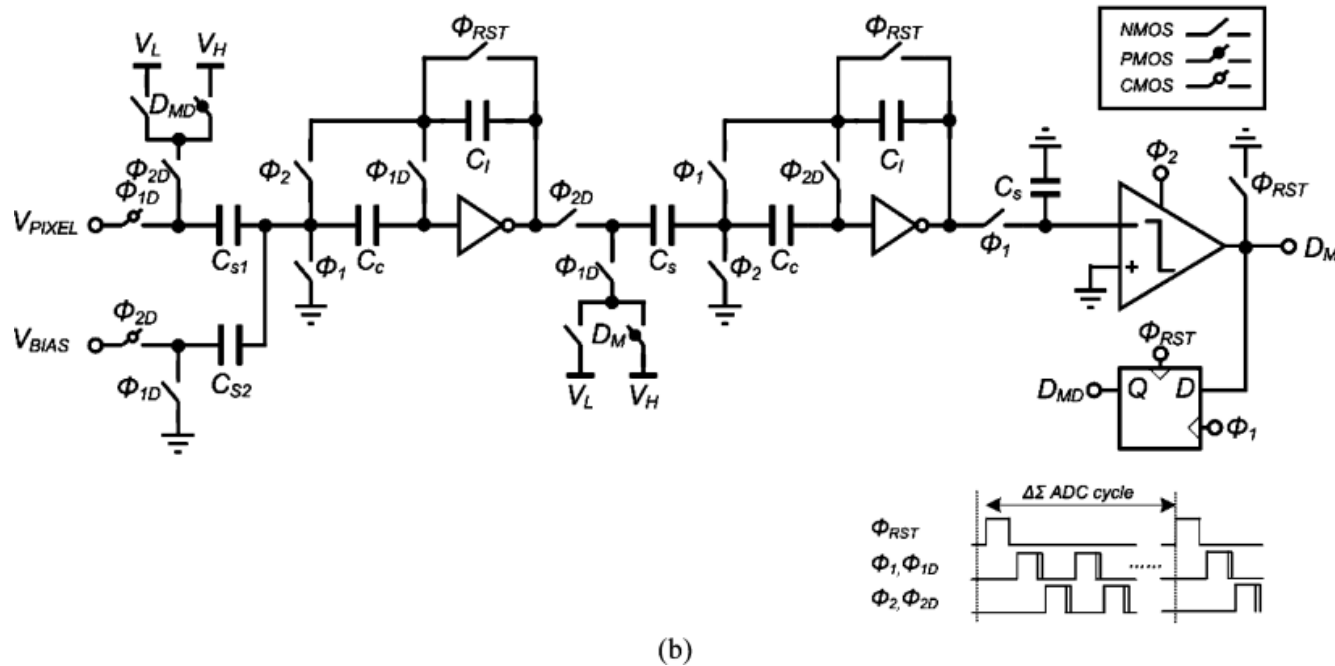


IDSM Circuit Model

Boris Murmann


bmurmann@hawaii.edu

Template Project

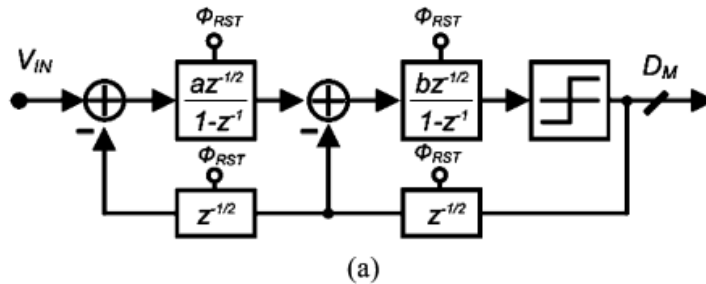

Y. Chae et al., "A 2.1 M Pixels, 120 Frame/s CMOS Image Sensor With Column-Parallel ADC Architecture," in IEEE Journal of Solid-State Circuits, Jan. 2011. <https://ieeexplore.ieee.org/document/5641589>

First Stab at Building an Integrator

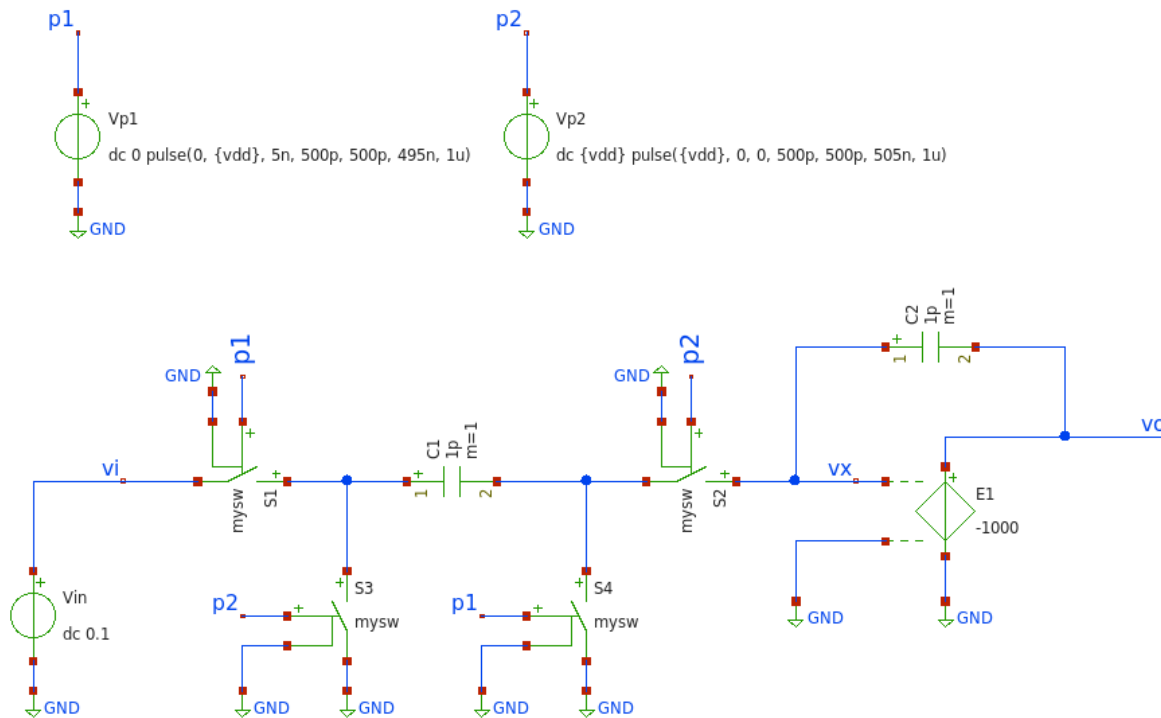

NGSPICE

```
.param temp=27 vdd=1.2
.model mysw SW vt={vdd/2} ron=10k roff=10gig
.control
save all
tran 1n 3u
plot vo
write tb_ideal_integ.raw
.endc
```

MODEL

```
.lib $::SG13G2_MODELS/cornerMOSlv.lib mos_tt
.lib $::SG13G2_MODELS/cornerRES.lib res_typ
```




Boris Murmann


/foss/designs/tb_ideal_integ.sch

2024-01-12 06:00:17

Non-overlapping two-phase clocks


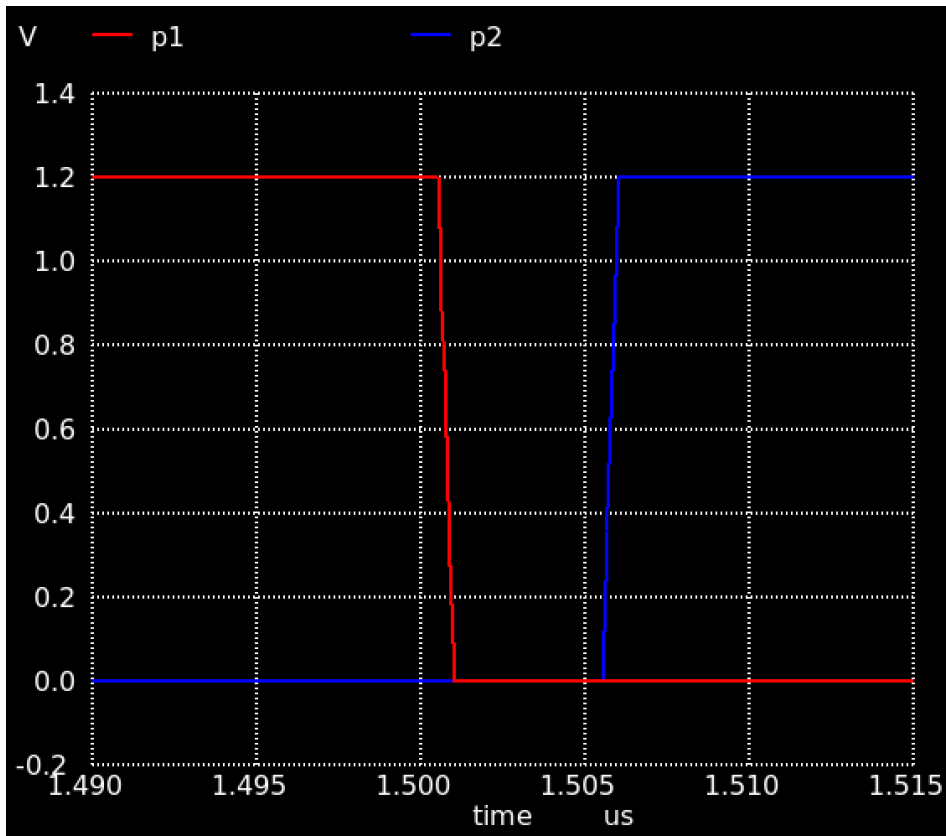


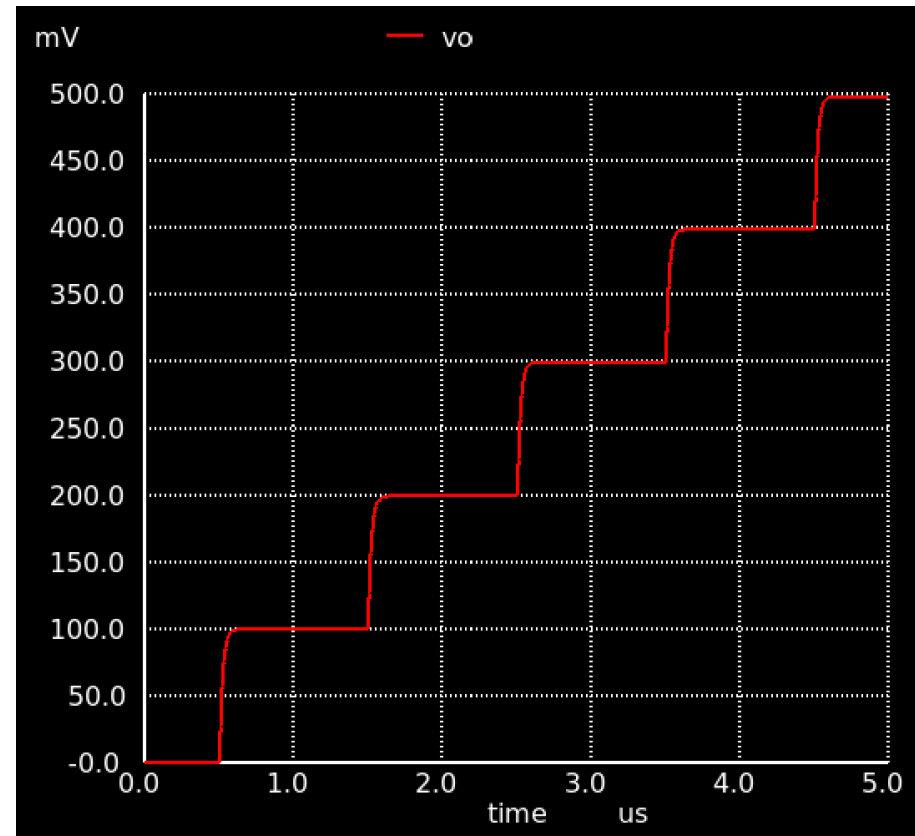Integrator output
(Amplifier gain = 1000)



Integrator Analysis (1)

Nonoverlapping clocks

  

t/T_s	Q_s	Q_f
$n-1$	$C_s \cdot V_i(n-1)$	$C_f \cdot V_o(n-1)$
$n-1/2$	0	$C_f \cdot V_o(n-1/2) = C_f \cdot V_o(n-1) + C_s \cdot V_i(n-1)$
n	$C_s \cdot V_i(n)$	$C_f \cdot V_o(n) = C_f \cdot V_o(n-1) + C_s \cdot V_i(n-1)$
$n+1/2$

Integrator Analysis (1)

- Assuming that V_o is sampled during ϕ_1 , we have


$$C_I V_o(n) = C_I V_o(n-1) + C_S V_i(n-1)$$

$$C_I V_o(z) = z^{-1} C_I V_o(z) + z^{-1} C_S V_i(z)$$

$$\therefore \frac{V_o(z)}{V_i(z)} = \frac{C_S}{C_I} \frac{z^{-1}}{1 - z^{-1}}$$

- This expression holds only for infinite amplifier gain
 - Let's look at impact of finite gain
 - Causes integrator gain error and leakage

Finite Gain (1)

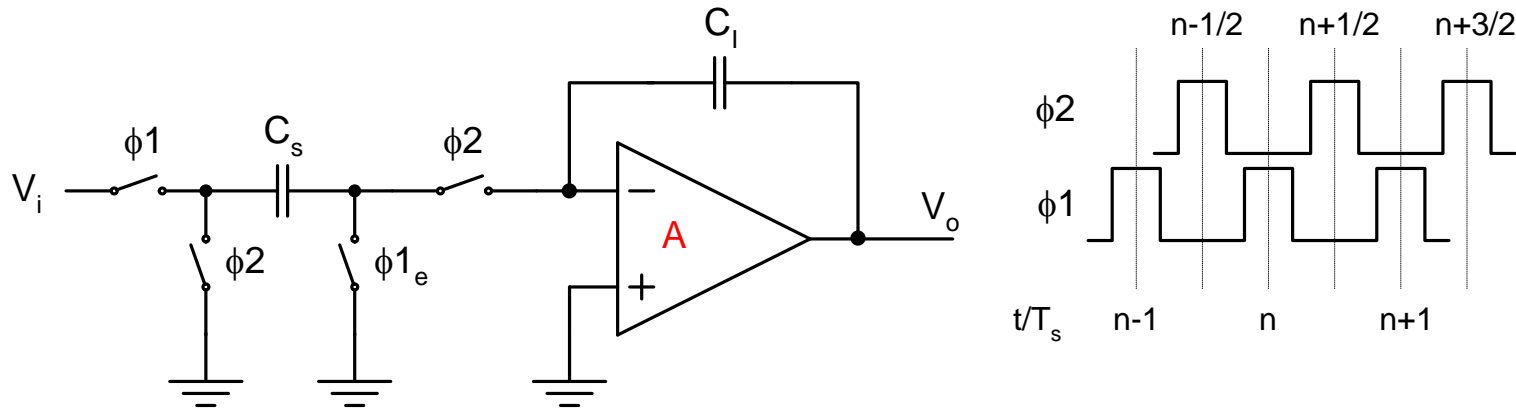

t/T_s	Q_s	Q_f
$n-1$	$C_s \cdot V_i(n-1)$	$C_f \cdot V_o(n-1) \cdot [1 + 1/A]$
$n-1/2$	$C_s \cdot V_o(n-1/2)/A$	$C_f \cdot V_o(n-1/2) \cdot [1 + 1/A] = C_f \cdot V_o(n-1) \cdot [1 + 1/A] + C_s \cdot V_i(n-1) - C_s \cdot V_o(n-1/2)/A$
n	$C_s \cdot V_i(n)$	$C_f \cdot V_o(n) \cdot [1 + 1/A] = C_f \cdot V_o(n-1) \cdot [1 + 1/A] + C_s \cdot V_i(n-1) - C_s \cdot V_o(n)/A$
$n+1/2$

Finite Gain (2)

- Again, assuming that V_o is sampled during ϕ_1 , we have



$$C_I V_o(z) \left[1 + \frac{1}{A} \right] = z^{-1} C_I V_o(z) \left[1 + \frac{1}{A} \right] + z^{-1} C_s V_i(z) - \frac{C_s}{A} V_o(z)$$

$$\therefore \frac{V_o(z)}{V_i(z)} \cong \frac{C_s}{C_I} \frac{z^{-1} \left(1 - \frac{1}{A} \left[1 + \frac{C_s}{C_I} \right] \right)}{1 - \left(1 - \frac{1}{A} \frac{C_s}{C_I} \right) z^{-1}} = \frac{g \cdot z^{-1}}{1 - [1 - \alpha] \cdot z^{-1}}$$


$$V_o(z) = [1 - \alpha] \cdot z^{-1} V_o(z) + g \cdot z^{-1} V_i(z)$$

- Finite gain results in "leaky integrator" (and gain error)
 - Some fraction of previous output is lost in new cycle

Integrator output
(Amplifier gain = 20)

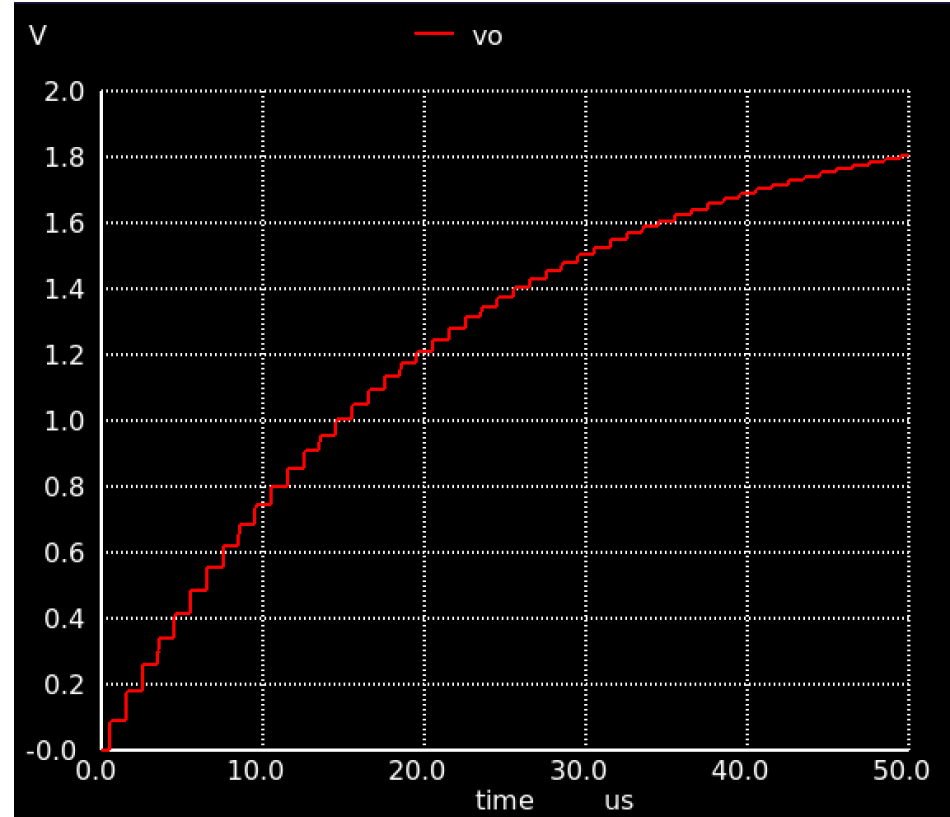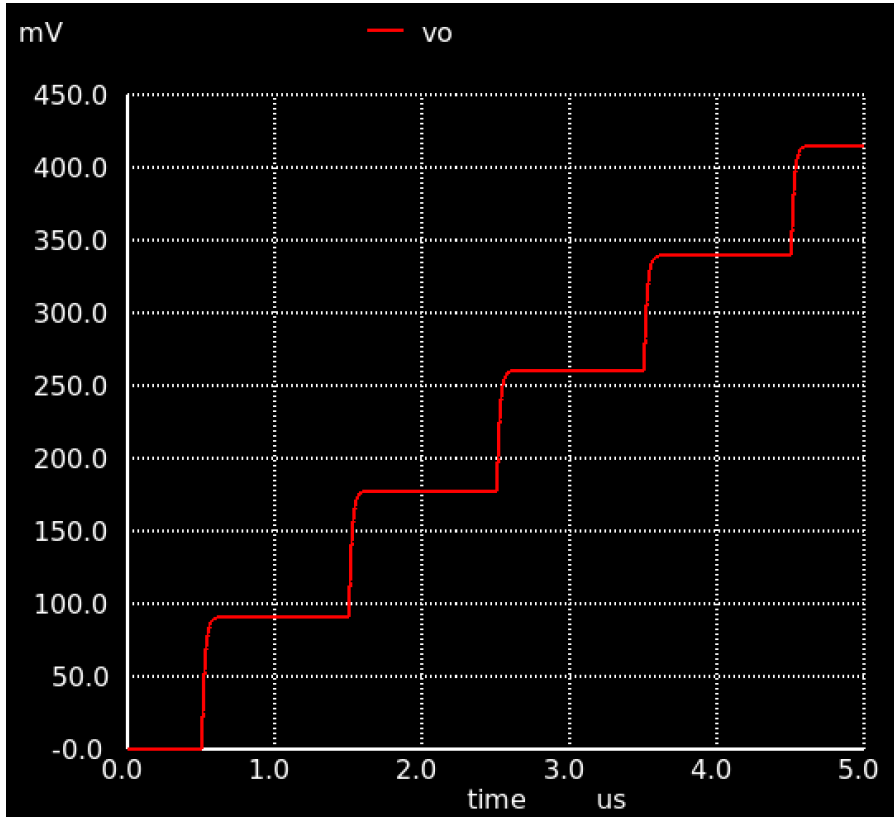

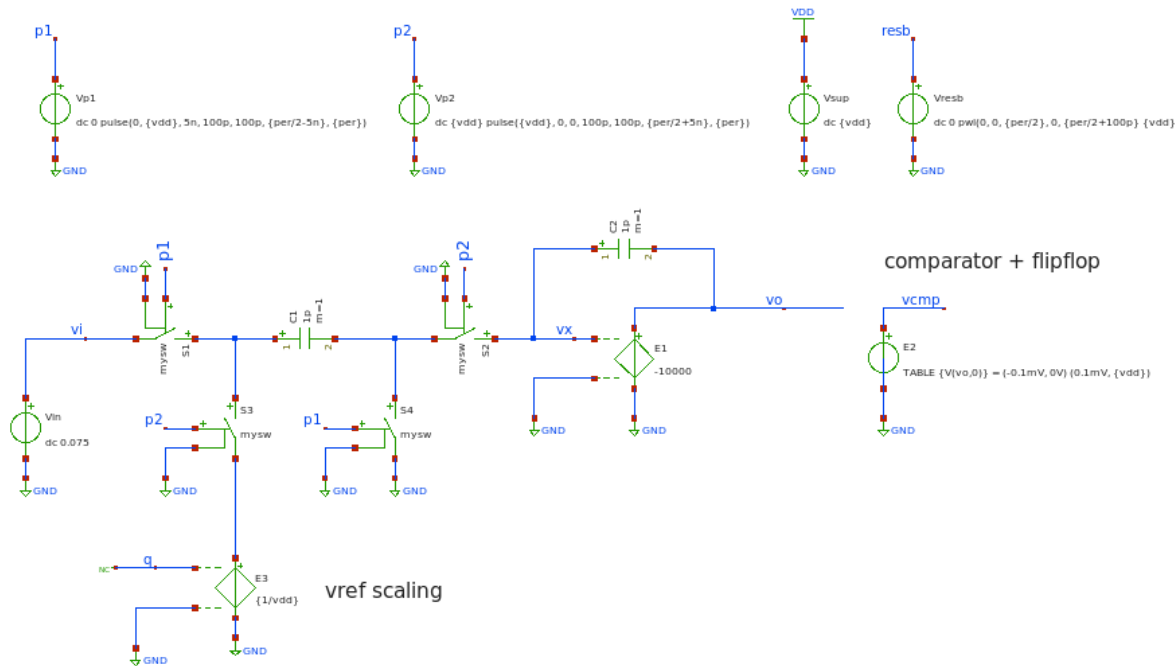First Stab at Building A First-Order Modulator



Flipflop from IHP library



NGSPICE

```
*DFF CLK D Q Q_N RESET_B VDD VSS
x1 p1 vcmp q qn resb VDD GND sg13g2_dfrbp_1
.param temp=27 vdd=1.2 per=1u
.model mysw SW vt={vdd/2} ron=10k roff=10gig
.option method=gear reltol=1e-4
```

```
.control
save all
tran 10n 64u
plot vo q
set wr_singlescale
set wr_vecnames
wrdata tb_ideal_idsm1.txt vo q p1 p2
.endc
```

MODEL

```
.lib $::SG13G2_MODELS/cornerMOSlv.lib mos_tt
.lib $::SG13G2_MODELS/cornerRES.lib res_typ
.inc /foss/pdks/sq13q2/libs.ref/sq13q2_stdcell/spice/sq13q2_stdcell.spice
```




Boris Murmann

```
/foss/designs/tb ideal idsm1.sch
```

2024-01-16 05:17:16

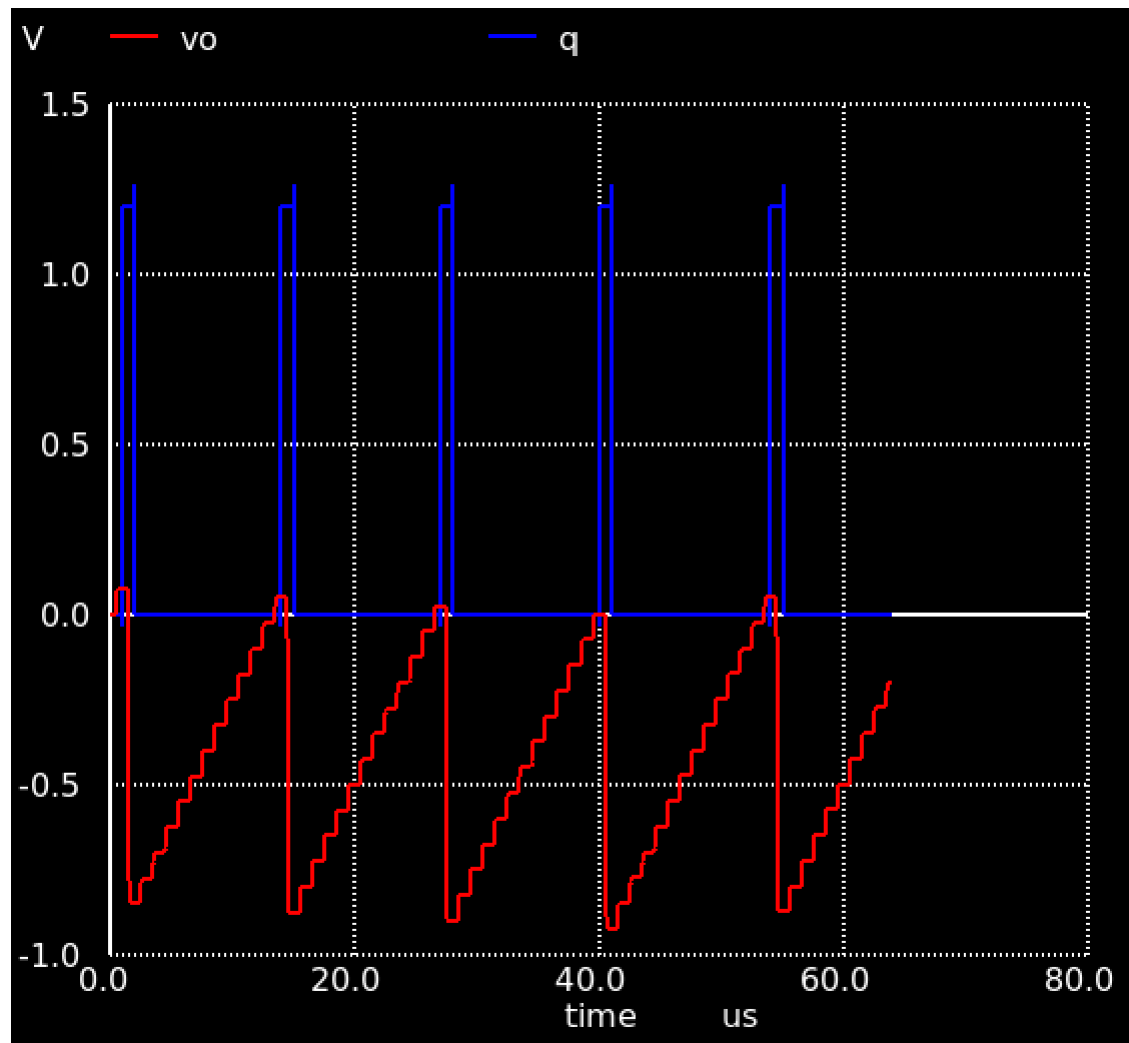Integrator output and feedback pulses match
behavioral simulation!



Next Steps

- Add second integrator (second-order modulator)
- Write some post-processing scripts
 - Detailed measurements
 - Emulate counters to create final digital output
- Increasingly “transistorize” the implementation
 - Shift voltages to practical levels (can’t have negative voltages)
 - MOSFET switches
 - Comparator
 - Inverter-based amplifier
 - With correlated double-sampling to achieve high gain