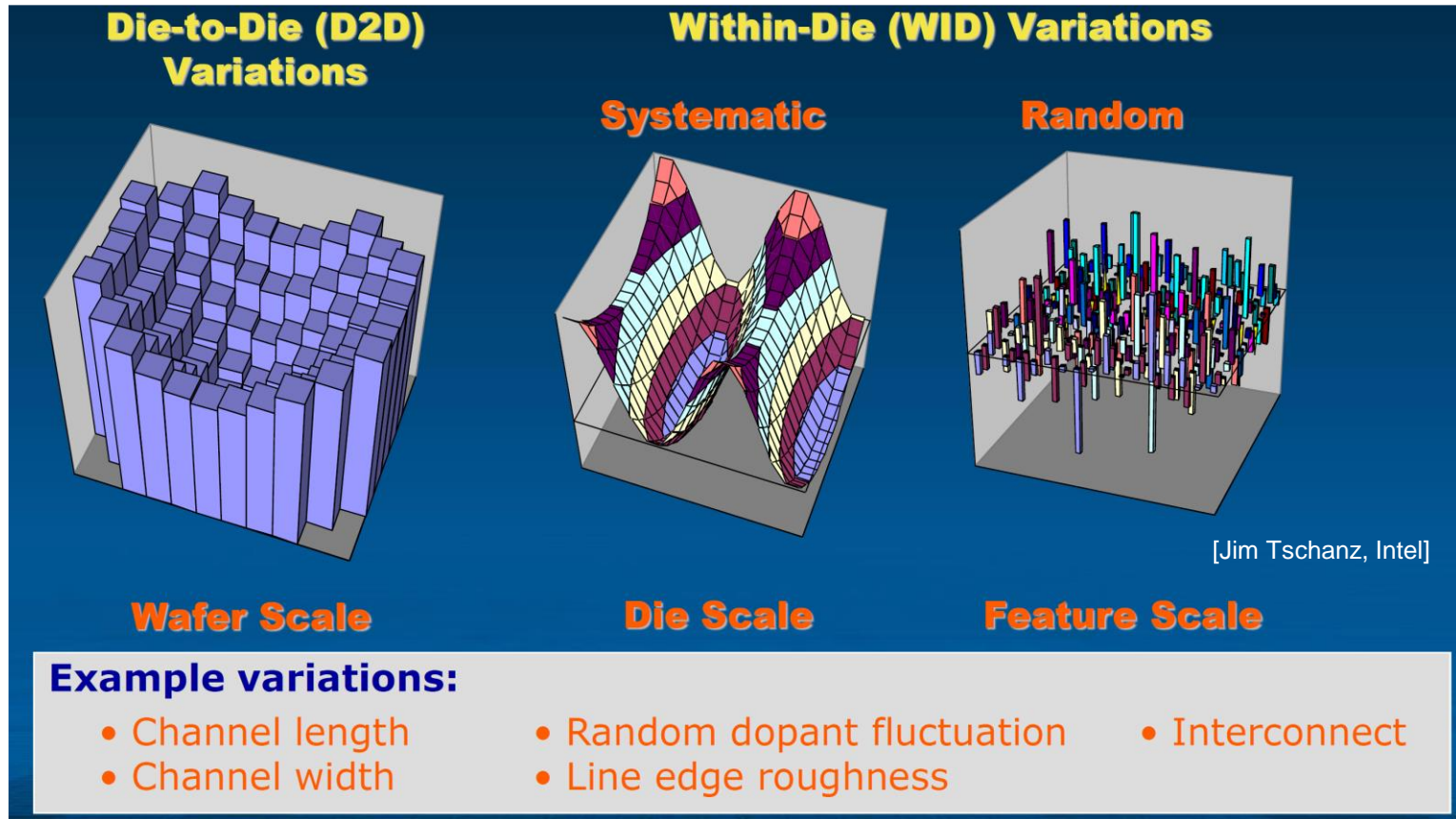


# Schematic & Layout Deliberations

**Boris Murmann**  
**[bmurmann@hawaii.edu](mailto:bmurmann@hawaii.edu)**


# Parameter Variations in Integrated Circuits




Affects all transistors (of the same type) in the same way

Causes differences between individual transistors (e.g.,  $V_t$ )

# Wafer-Level Variations

 

 Wafer made yesterday  
 All NMOS are “slow”  
 All PMOS are “nominal”  
 All R are nominal  
 All C are “fast”



Wafer made today  
 All NMOS are “fast”  
 All PMOS are “fast”  
 All R are nominal  
 All C are “slow”

Examples:

Parameter	“Slow”	“Nominal”	“Fast”
$V_t$	0.4V	0.3V	0.2V
$\mu C_{ox}$ (NMOS)	240 mA/V <sup>2</sup>	300 mA/V <sup>2</sup>	360 mA/V <sup>2</sup>
$\mu C_{ox}$ (PMOS)	80 mA/V <sup>2</sup>	100 mA/V <sup>2</sup>	120 mA/V <sup>2</sup>
$R_{poly}$	60Ω/□	50Ω/□	40Ω/□
$R_{nwell}$	1.4 kΩ/□	1 kΩ/□	0.6 kΩ/□
$C_{MIM}$	1.15 fF/mm <sup>2</sup>	1 fF/mm <sup>2</sup>	0.85 fF/mm <sup>2</sup>

## 2.1 NMOS

$V_{GS} \leq 1,65 \text{ V @ } 125^\circ\text{C}$

Parameter	Name	Unit	Min	Target	Max	Meas. Cond.	Comment
Threshold Voltage Short Channel Device	VTN10x013	V	0.43	0.50	0.55	A.a1	WxL = 10 x 0.13 $\mu\text{m}^2$
Threshold Voltage Long Channel Device	VTN10x10	V	0.16	0.20	0.24	A.a1	WxL = 10 x 10 $\mu\text{m}^2$
Threshold Voltage Small Channel Device	VTN015x013	V	0.4	0.54	0.68	A.a1	WxL = 0.15 x 0.13 $\mu\text{m}^2$
Saturation Current Short Channel Device	IDSN013	$\mu\text{A}/\mu\text{m}$	380	480	600	A.b1	WxL = 10 x 0.13 $\mu\text{m}^2$
Off-Current Short Channel Device	IOFFN013	LOG10 (A/ $\mu\text{m}$ )		-10	-9	A.c1	WxL = 10 x 0.13 $\mu\text{m}^2$
Drain Induced Barrier Lowering 0.1/1.2V	DIBLN013	mV/V	20	50	80	A.d1	WxL = 10 x 0.13 $\mu\text{m}^2$
Sub Threshold Slope	SSN013	mV/dec	76	82	88	A.e	WxL = 10 x 0.13 $\mu\text{m}^2$

## 2.12 MIM Capacitor

Parameter	Name	Unit	Min	Target	Max	Meas. Cond.	Comment
Specific Area Capacitance	CMIMA	fF/ $\mu\text{m}^2$	1.35	1.5	1.65	A.k	
Specific Capacitance MIM Perimeter	CMIMP	aF/ $\mu\text{m}$		40		A.l	
Breakdown Voltage	BVMIM	V	15	23		A.y	
Voltage Coefficients	VCMIM1 VCMIM2	ppm/V ppm/V <sup>2</sup>		-26 5		A.ah	
Temperature Coefficient	TCMIM1 TCMIM2	ppm/K ppm/K <sup>2</sup>		3.6 0.002		A.ad	
Matching Coefficient	KCMIM	nm					


[https://github.com/IHP-GmbH/IHP-Open-PDK/blob/main/ihp-sg13g2/libs.doc/doc/SG13G2\\_os\\_process\\_spec.pdf](https://github.com/IHP-GmbH/IHP-Open-PDK/blob/main/ihp-sg13g2/libs.doc/doc/SG13G2_os_process_spec.pdf)

# Characterization Across “Corners”

Corner T = −20 °C	TT	FF	FS	SF	SS
V <sub>out</sub> (mV)	244.4	248.6	229.7	264.7	249.3
I <sub>DD</sub> (nA)	256	475	243	227	104
DC Gain (dB)	49.8	52	50	50.4	47.4
UGF (MHz)	0.67	1.58	0.63	0.59	0.22
PM (degrees)	69.2	64.6	69	69.9	76.9
PSRR+ (dB)	54.4	56.7	54.7	55.2	52
PSRR- (dB)	56.9	58.9	57.1	57.4	54.7
1% Ts+/Ts- (ns)	685/438	272/182	566/337	854/336	2632/880
Corner T = 27 °C	TT	FF	FS	SF	SS
V <sub>out</sub> (mV)	249.9	244.5	249.3	249.9	250
I <sub>DD</sub> (nA)	488	579	505	479	485
DC Gain (dB)	51.3	51.7	52.1	50.4	51
UGF (MHz)	1.09	1.68	1.13	1.08	0.88
PM (degrees)	69.2	64.3	69.5	69	73.1
PSRR+ (dB)	56.1	56.7	56.9	55.2	55.7
PSRR- (dB)	58.2	58.5	59.8	58.9	58.3
1% Ts+/Ts- (ns)	520/319	240/207	506/322	519/321	719/490
Corner T = 80 °C	TT	FF	FS	SF	SS
V <sub>out</sub> (mV)	255.8	249.1	233.9	277.1	259.8
I <sub>DD</sub> (nA)	1177	2417	1338	1061	621
DC Gain (dB)	52.6	53	53	52.1	51.5
UGF (MHz)	2.2	5.68	2.5	1.98	0.97
PM (degrees)	74.3	77.3	75.8	73.3	73.4
PSRR+ (dB)	57.4	57.7	57.9	56.7	56.3
PSRR- (dB)	59.4	59.7	59.8	58.9	58.4
1% Ts+/Ts- (ns)	356/235	130/123	230/239	233/210	838/436

- Complexity explodes very quickly
  - E.g., 5 (process) x 3 (temperature) x 3 (supply voltage) = 45 tests!

# Stage Testbench

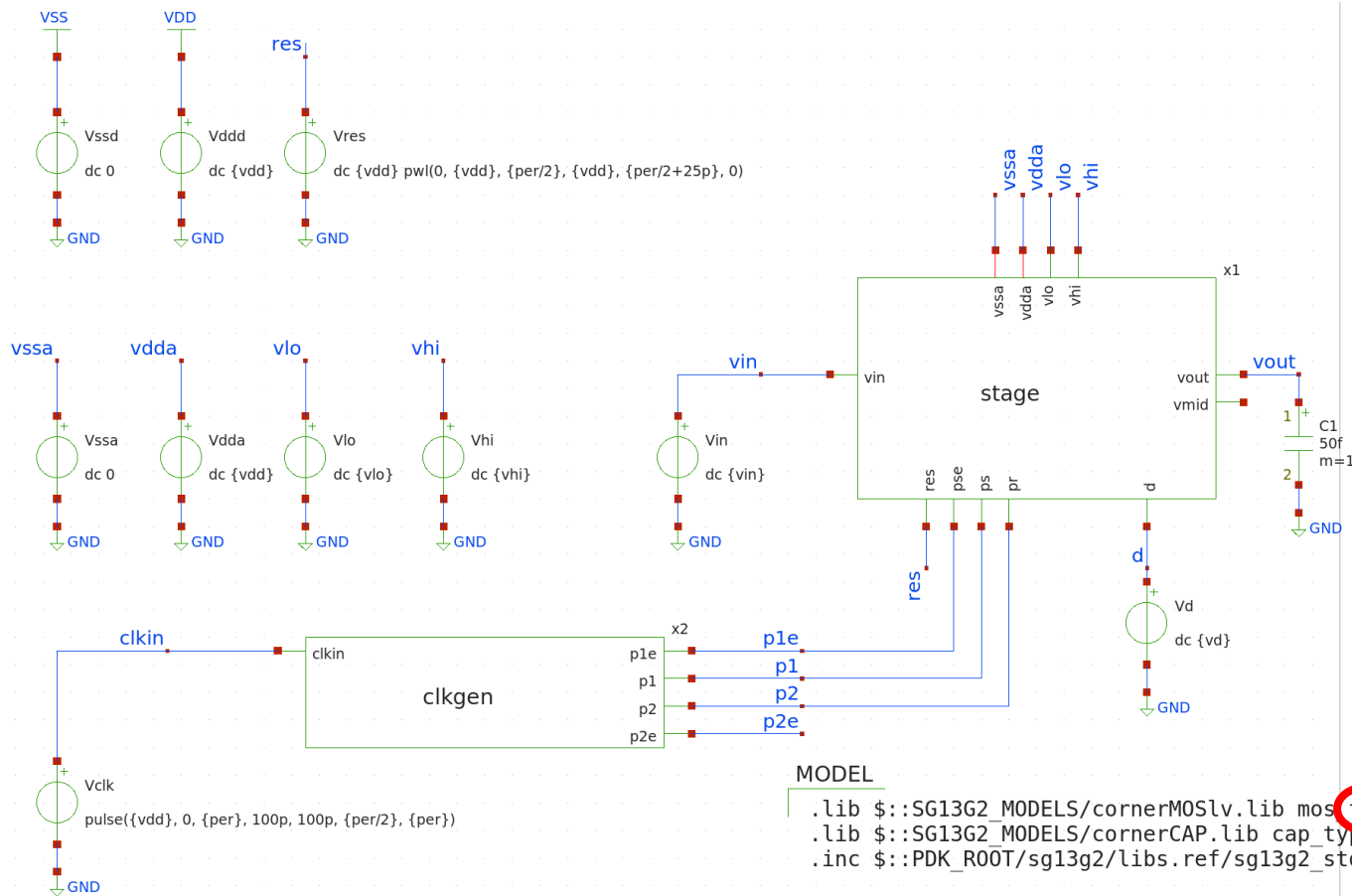

NGSPICE

```
.param temp=27 per=20n vdd=1.2
.param vin=0.6 vlo=0.3 vhi=0.9 vd={vdd}
.option method=gear reltol=1e-4
```

```
.control
set wr_singlescale
set wr_vecnames
set color0 = white
tran 100p 60n
plot p2e vout
***
wrdata tb_stage_corners_tt.txt p2e vout
***
.endc
```

**tt, ss, ff**

## MODEL



```
.lib $::SG13G2_MODELS/cornerMOSlv.lib mos tt
.lib $::SG13G2_MODELS/cornerCAP.lib cap typ
.inc $::PDK_ROOT/sg13g2/libs.ref/sg13g2_stdcell/spice/sg13g2_stdcell.spice
```



# Boris Murmann

/foss/designs/tb\_stage\_corners.sch

2024-04-03 03:06:35

  


Next stage samples here

- How close to the “final value” are we at the sampling instant?
  - This is called the dynamic settling error (measured in percent)
- How does the dynamic settling error across corners?
- Need to slow down clock frequency to measure final value (e.g., 4x)

 
## Output with per = 80ns

[https://github.com/bmurmnn/EE628/blob/main/5\\_Design/3\\_Real\\_circuits/tb\\_stage\\_corners.ipynb](https://github.com/bmurmnn/EE628/blob/main/5_Design/3_Real_circuits/tb_stage_corners.ipynb)





 
## Zooming Into 2<sup>nd</sup> Redistribution Phase


 
# Dynamic Error

$$\text{Error} = (\text{value}(t) - \text{final}) / \text{final}$$



# Dynamic Error on Log Scale

0.1%-settling time  $\sim 8, 11, 13$  ns (ff, tt, ss)

Max clock frequency for slow corner  $\sim 1/(2 \cdot 13\text{ns}) = 38.5$  MHz

