



# Comparator

**Boris Murmann**  
**[bmurmann@hawaii.edu](mailto:bmurmann@hawaii.edu)**

## Next Steps


- Add second integrator (second-order modulator)
- Write some post-processing scripts
  - Detailed measurements
  - Emulate counters to create final digital output
- Increasingly “transistorize” the implementation
  - Shift voltages to practical levels (can’t have negative voltages)
  - **Comparator**
  - Inverter-based amplifier with CDS
  - MOSFET switches & clock generator

# Template Circuit

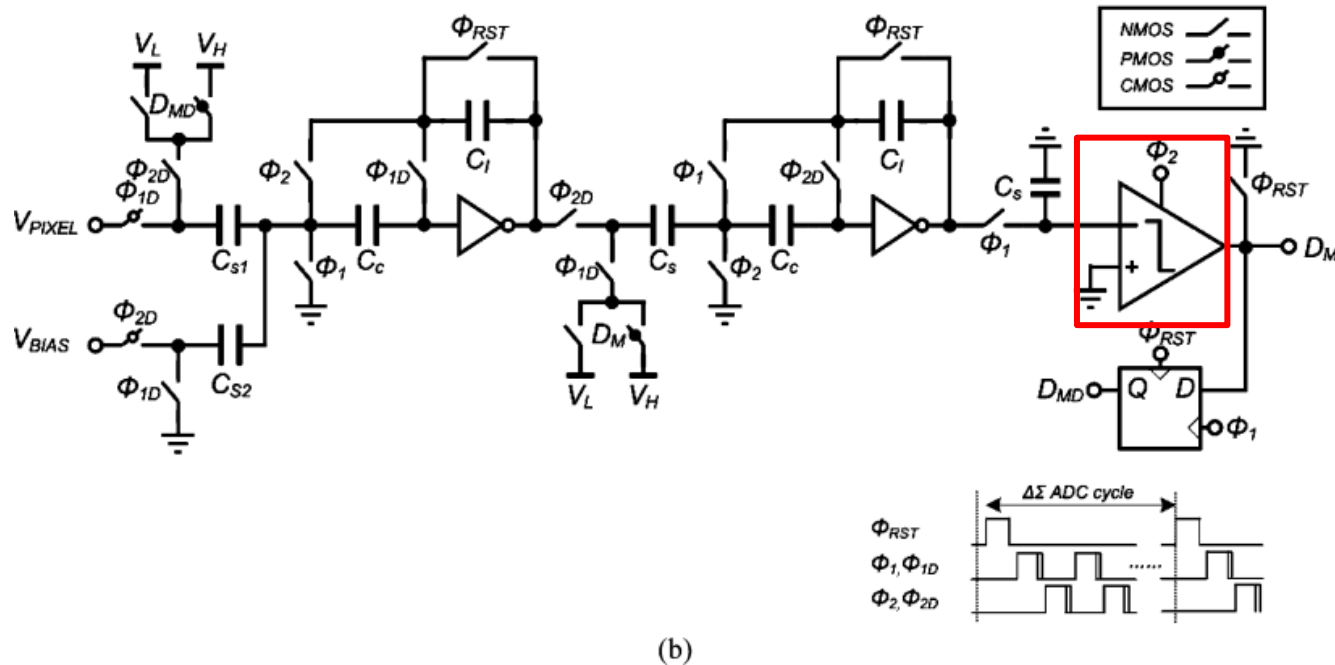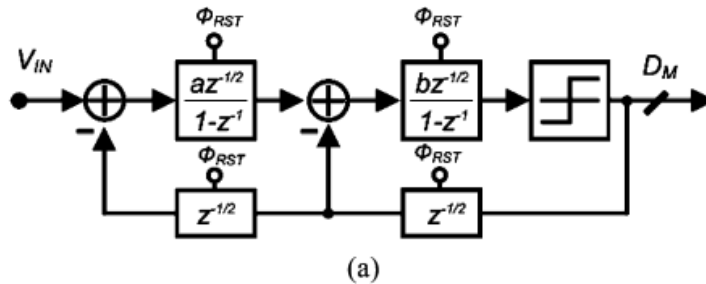


Y. Chae et al., "A 2.1 M Pixels, 120 Frame/s CMOS Image Sensor With Column-Parallel ADC Architecture," in IEEE Journal of Solid-State Circuits, Jan. 2011. <https://ieeexplore.ieee.org/document/5641589>

# Current Model Schematic (IDSM2)

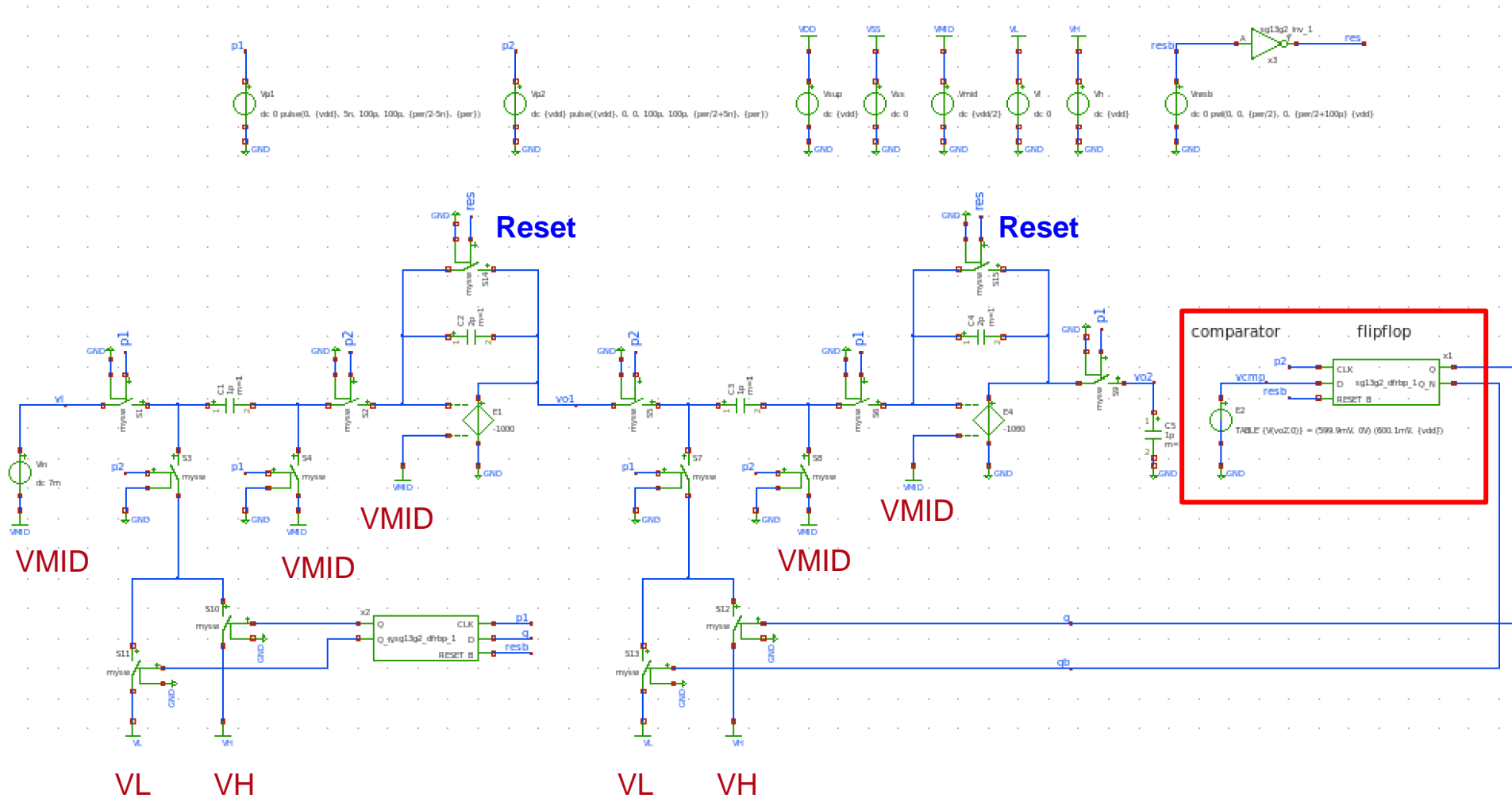



# Circuit Used in The Original Template Design

The marked devices should be NMOS

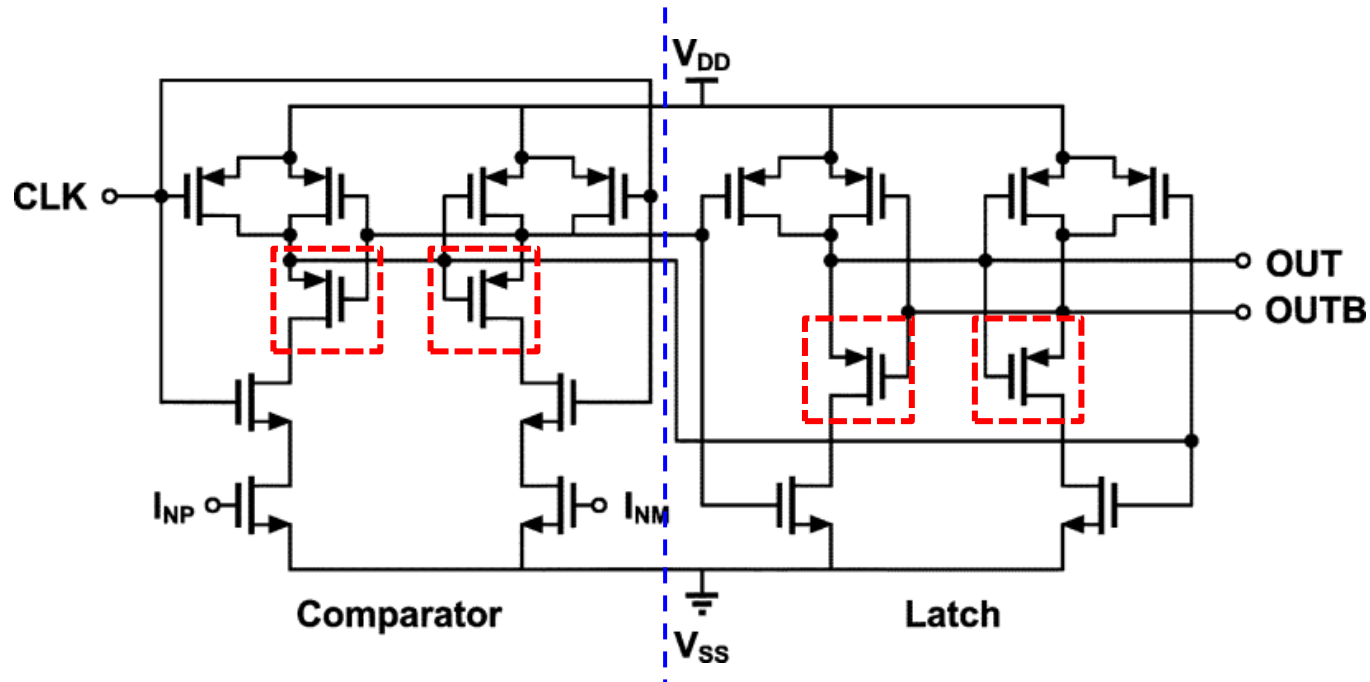

Y. Chae and G. Han, "Low Voltage, Low Power, Inverter-Based Switched-Capacitor Delta-Sigma Modulator," in IEEE Journal of Solid-State Circuits, Feb. 2009.  
<https://ieeexplore.ieee.org/abstract/document/4768910>



# Ideal Voltage Comparator

  

- Function

- Compare the values of two analog voltages (e.g., an input signal and a reference voltage) and generate a digital 1 or 0 indicating the polarity of the difference

  
# The Fastest Way to Find the Polarity Comparison: Latch Circuit



The slightest imbalance will push the circuit out of the metastable state and latch to one of the stable states

# Detailed Analysis

Conceptual Circuit

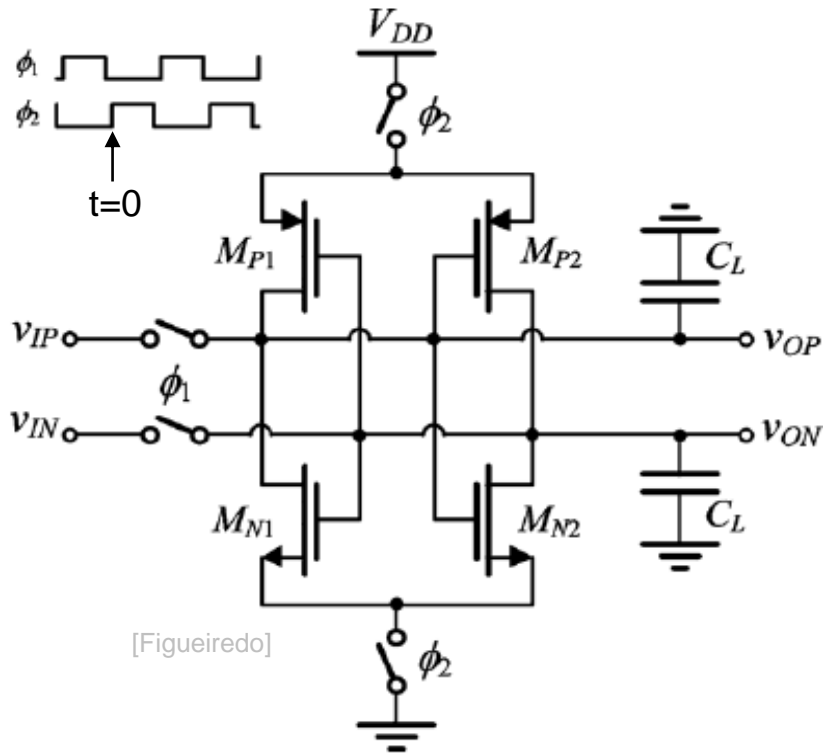

$\phi_1$ : Set up initial condition ( $v_{OD0}$ )  
 $\phi_2$ : Enable positive feedback

$$G_m = g_{mN} + g_{mP} \quad \text{Inverter Transconductance}$$

$$\frac{dv_{OP}}{dt} = \frac{i_1(t)}{C_L} = -\frac{G_m v_{ON}(t)}{C_L}$$

$$\frac{dv_{ON}}{dt} = \frac{i_2(t)}{C_L} = -\frac{G_m v_{OP}(t)}{C_L}$$

$$\tau = \frac{C_L}{G_m}$$

$$v_{OD}(t) = v_{OP}(t) - v_{ON}(t)$$


$$v_{OD}(t) = v_{OD0} \cdot e^{t/\tau}$$

$$A(t) = \frac{v_{OD}(t)}{v_{OD0}} = e^{t/\tau}$$



 
# Transient Response

Nodes  $v_{OP}$  and  $v_{ON}$  for differential inputs of 1mV, 1 $\mu$ V, 1nV and 1pV


 
# Transient Response of Voltage Difference (Log Scale)




$$v_{OD1} = v_{OD0} \cdot e^{t_1/\tau}$$


$$v_{OD2} = v_{OD0} \cdot e^{t_2/\tau}$$

$$\tau = \frac{t_2 - t_1}{\ln\left(\frac{v_{OD2}}{v_{OD1}}\right)} = \frac{600\text{ps}}{\ln(10^6)} = \frac{600\text{ps}}{6 \cdot 2.3} = 43\text{ps}$$

## Another Way to Dial in Imbalance

 

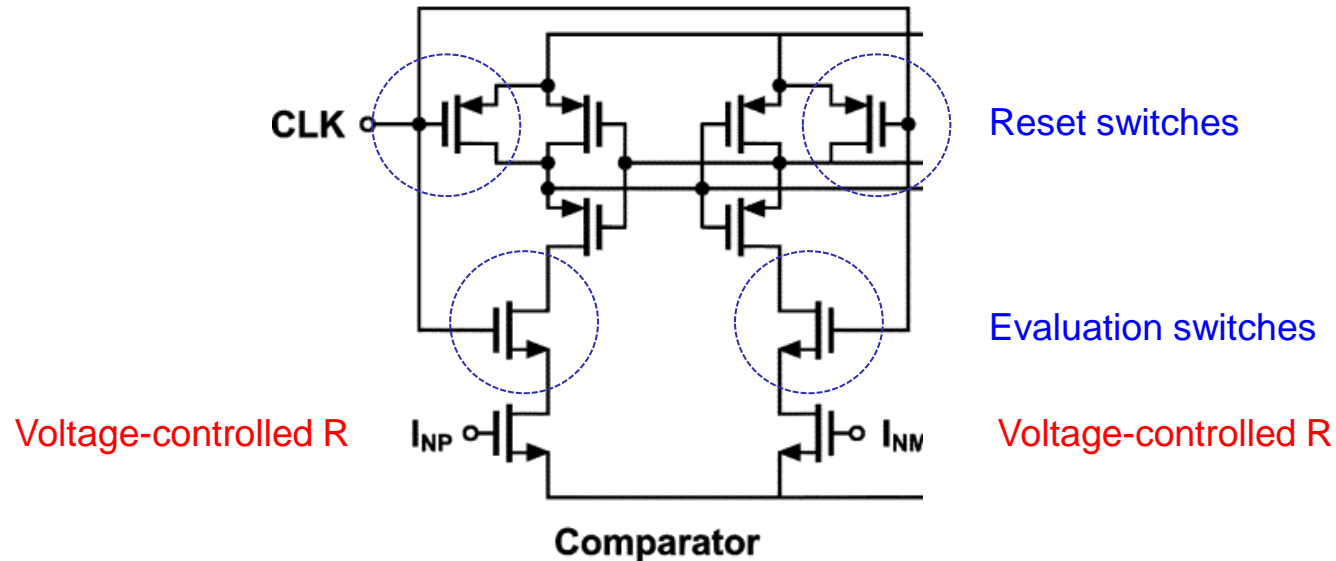
# Circuit Used in The Original Template Design



Y. Chae and G. Han, "Low Voltage, Low Power, Inverter-Based Switched-Capacitor Delta-Sigma Modulator," in IEEE Journal of Solid-State Circuits, Feb. 2009.  
<https://ieeexplore.ieee.org/abstract/document/4768910>

# Prototype Circuit

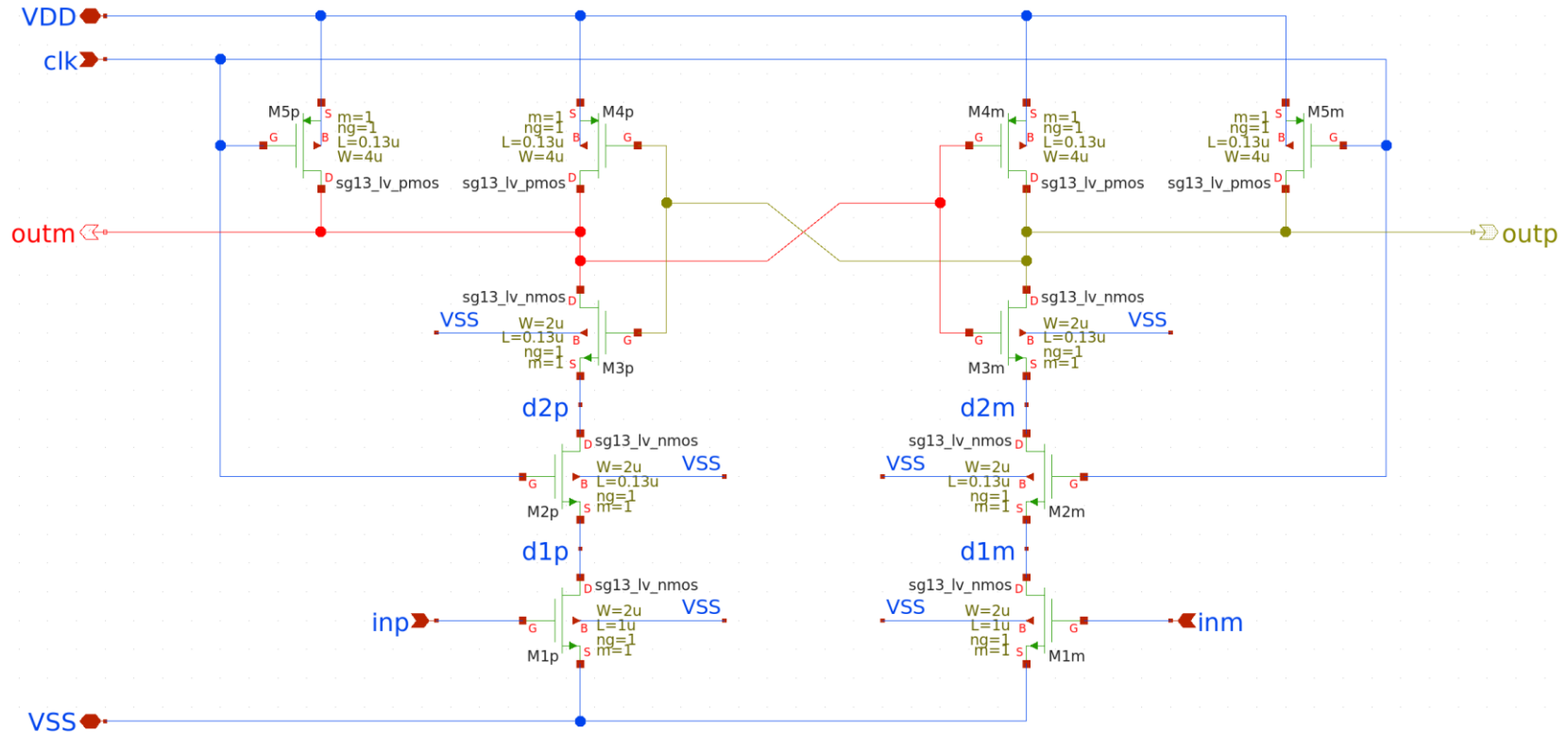

**XSCHEM**

Boris Murmann  
x1. /foss/designs/comp.sch

2024-01-26 23:04:10

# Testbench


## NGSPICE

```
.param temp=27 vdd=1.2 per=1u vdifff=1m
.option method=gear reltol=1e-5

.control
save all
tran 10p 4n
alterparam vdifff=1u
reset
tran 10p 4n
plot clk tran1.outm tran1.outp tran2.outm tran2.outp
.endc
```
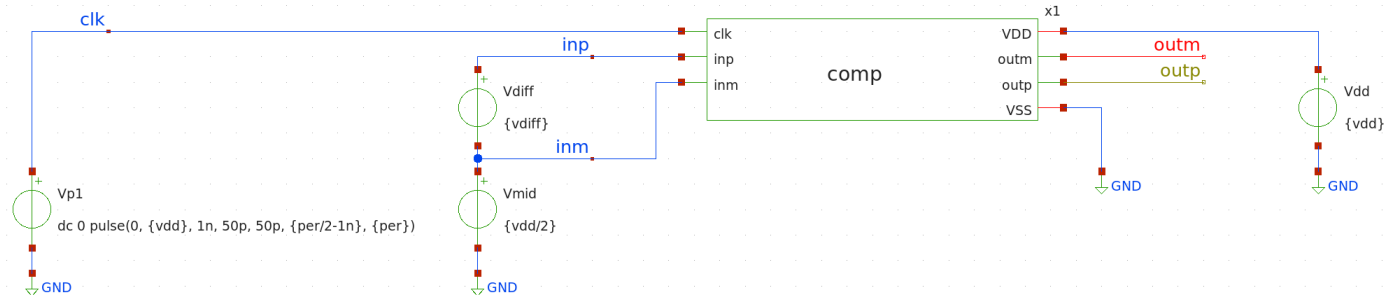
## MODEL


```
.lib $::SG13G2_MODELS/cornerM0S1v.lib mos_tt
```




Boris Murmann  
/foss/designs/tb\_comp

2024-01-27 00:04:56

# Simulation Result

 

# Alternative (Classical) Implementation

 

## “Strong ARM Latch”

Madden & Bowhill, US Patent 4910713,  
Mar. 20, 1990


First journal paper:  
[Kobayashi et al., JSSC, Apr. 1993]

“Strong ARM” paper:  
[Montanaro, Madden et al., JSSC, Nov. 1996]

B. Razavi, "The StrongARM Latch [A Circuit for All Seasons]," in IEEE Solid-State Circuits Magazine, Spring 2015. <https://ieeexplore.ieee.org/abstract/document/7130773>



 
## General Issue for all Implementations: Offset Voltage



- Biases the decision in one direction

# Offset in a StrongARM Latch

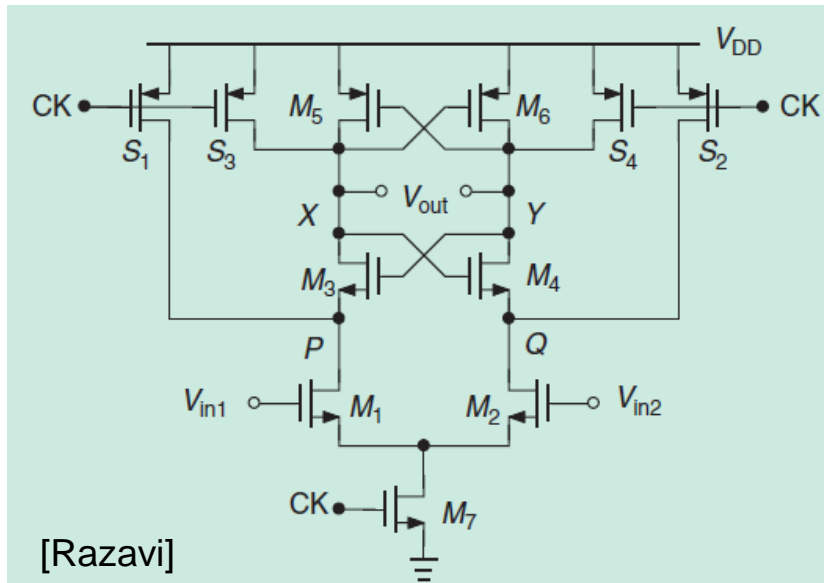

- Static offset due to  $V_t$  mismatch in input pair
- Other mismatch sources attenuated by gain from initial amplification phase


$$\sigma_{VOS,stat} \approx \frac{A_{VT}}{\sqrt{W_1 L_1}} \quad \text{Pelgrom's formula}$$

- Dynamic offset due to mismatch in  $C_P$  and  $C_Q$

$$V_{OS,dyn} \approx \frac{V_{tn}}{2} \left( \frac{C_P}{C_Q} - \frac{C_Q}{C_P} \right) = V_{tn} \frac{\Delta C}{C}$$

$$\text{Example: } 500mV \cdot 5\% = 25mV$$

Amplification phase:

 

## Kickback

 


Figure from [Figueiredo, TCAS2, July 2006]