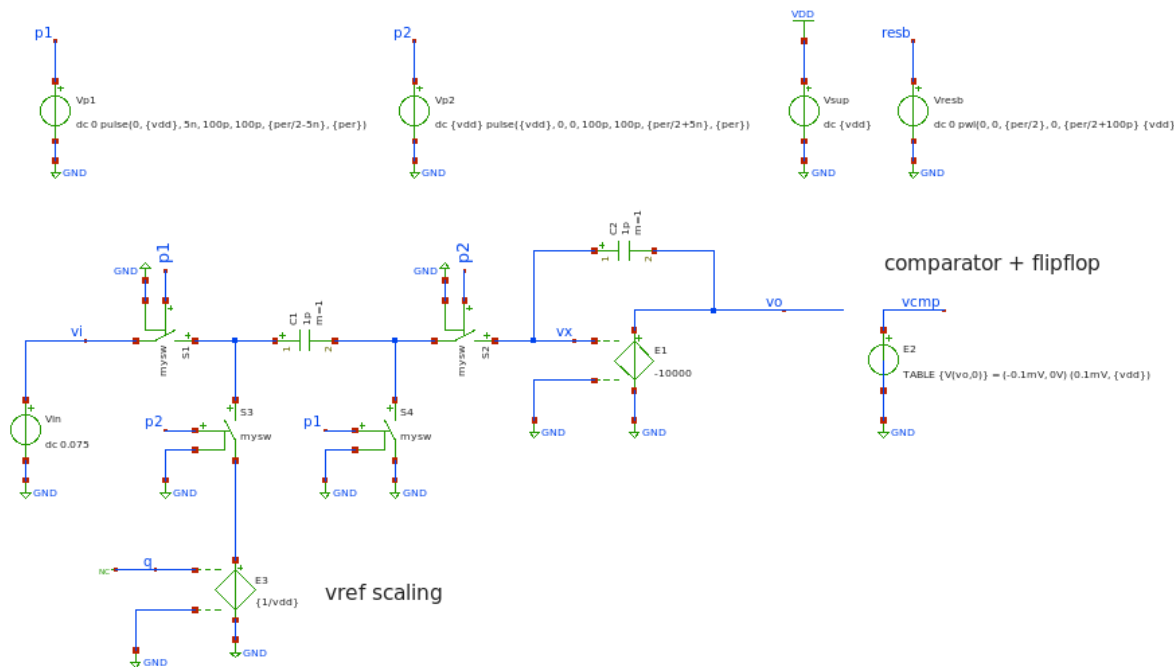


IDSM2 Circuit Model

Boris Murmann

bmurmann@hawaii.edu

IDSM1 Circuit Model



Flipflop from IHP library
(netlist instantiation)

NGSPICE

```
*DFF CLK D Q Q_N RESET_B VDD VSS
x1 p1 vcmp q qn resb VDD GND sg13g2_dfrbp_1
.param temp=27 vdd=1.2 per=1u
.model mysw SW vt={vdd/2} ron=10k roff=10gig
.option method=gear reltol=1e-4
```

```
.control
save all
tran 10n 64u
plot vo q
set wr_singlescale
set wr_vecnames
wdata tb_ideal_idsm1.txt vo q p1 p2
.endc
```

MODEL

```
.lib $::SG13G2 MODELS/cornerMOSlv.lib mos_tt
.lib $::SG13G2 MODELS/cornerRES.lib res_typ
.inc /foss/pdks/sg13g2/libs.ref/sg13g2_stdcell/spice/sg13g2_stdcell.spice
```



Boris Murmann
/foss/designs/tb_ideal_idsm1.sch

2024-01-16 05:17:16

Fixing the IHP Standard Cell Symbols

- Start the container as root

```
docker exec -u root -t -i iic-osic-tools_xserver_uid_1000 /bin/bash
```

- Go to directory containing the IHP standard cell symbols

```
cd /foss/pdks/sg13g2/libs.tech/xschem/sg13g2_stdcells
```


- Run this command to fix the symbols' pin order (courtesy Mitch Bailey)

```
sed -i \  
-e 's/@VGND @VNB @VPB @VPWR/@VDD @VSS/' \  
-e 's/VGND=VGND VNB=VNB VPB=VPB VPWR=VPWR/VDD=VDD VSS=VSS/' \  
-e 's/VGND VNB VPB VPWR/VDD VSS/' \  
-e 's/@VDD @VSS @@Q @@Q_N/@@Q @@Q_N @VDD @VSS/' *
```

- This still doesn't completely fix the flipflop cell. Using a text editor, move "RESET_B" to the location shown below in in sg13g2_dfrbp_1.sym

```
format="@name @@CLK @@D @@Q @@Q_N @@RESET_B @VDD @VSS @prefix\\\\\\dfrbp_1"
```

First-Order Modulator with DFF Symbol

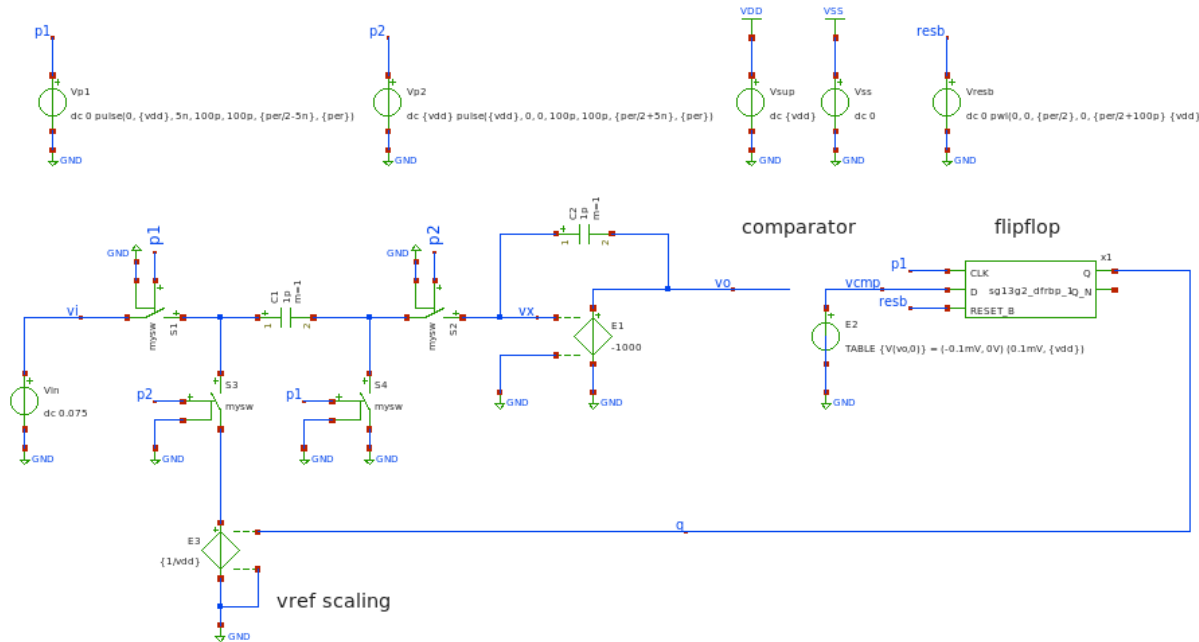

NGSPICE

```
.param temp=27 vdd=1.2 per=1u
.model mysw SW vt={vdd/2} ron=10k roff=10gig
.option method=gear reltol=1e-4

.control
save all
tran 10n 64u
plot vo q
set wr_singlescale
set wr_vecnames
wrdata tb_ideal_idsm1.txt vo q p1 p2
.endc
```

MODEL

```
.lib $::SG13G2_MODELS/cornerM0Slv.lib mos_tt
.lib $::SG13G2_MODELS/cornerRES.lib res_typ
.inc /foss/pdks/sg13g2/libs.ref/sg13g2_stdcell/spice/sg13g2_stdcell
```




Boris Murmann
/foss/designs/tb_ideal_idsm1.sch

2024-01-21 19:08:18

Next Steps


- Add second integrator (second-order modulator)
- Write some post-processing scripts
 - Detailed measurements
 - Emulate counters to create final digital output
- Increasingly “transistorize” the implementation
 - Shift voltages to practical levels (can’t have negative voltages)
 - Comparator
 - Clock generator
 - MOSFET switches
 - Inverter-based amplifier
 - With correlated double-sampling to achieve high gain

Template Circuit

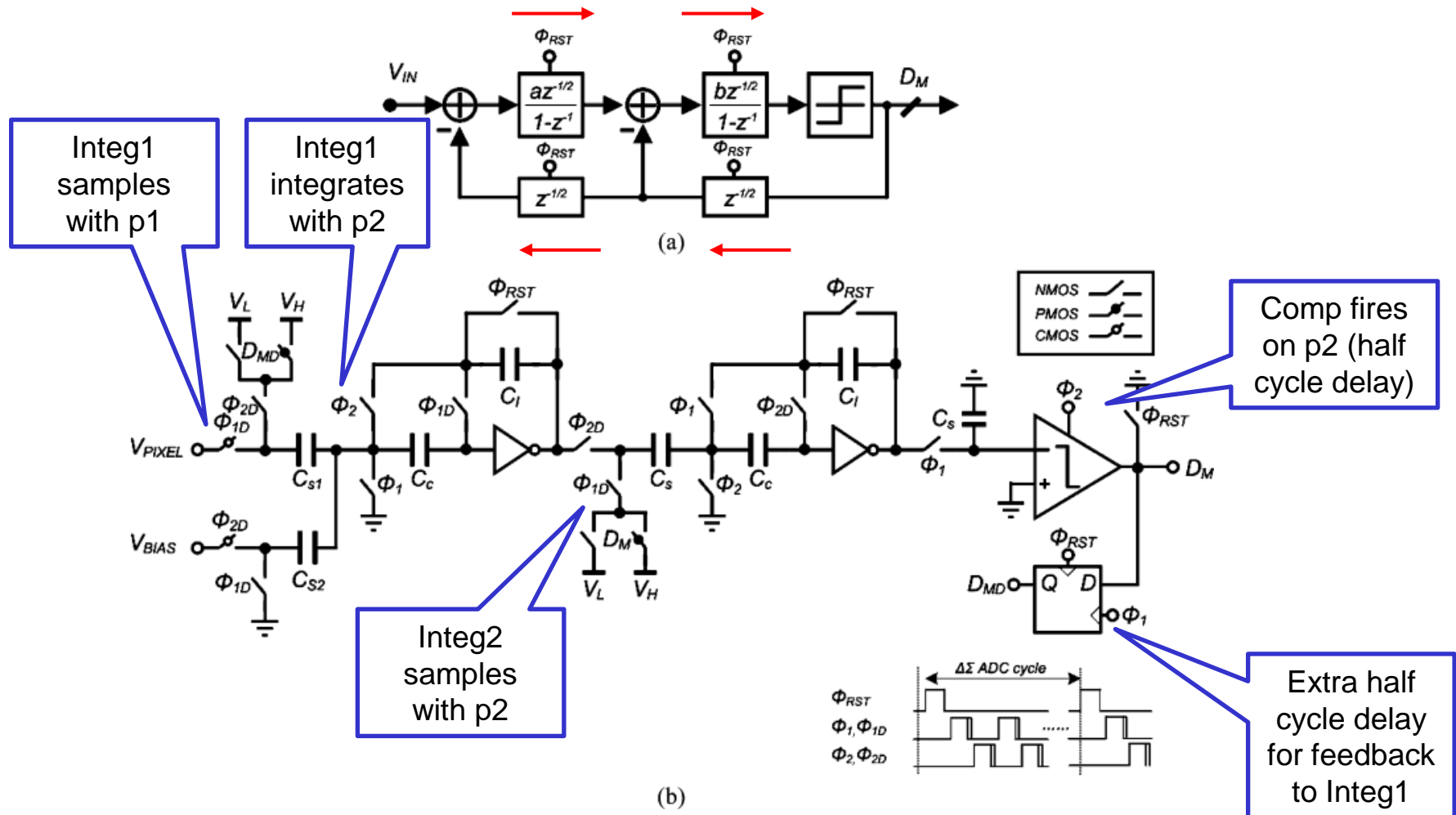


Y. Chae et al., "A 2.1 M Pixels, 120 Frame/s CMOS Image Sensor With Column-Parallel ADC Architecture," in IEEE Journal of Solid-State Circuits, Jan. 2011. <https://ieeexplore.ieee.org/document/5641589>

Second-Order Modulator

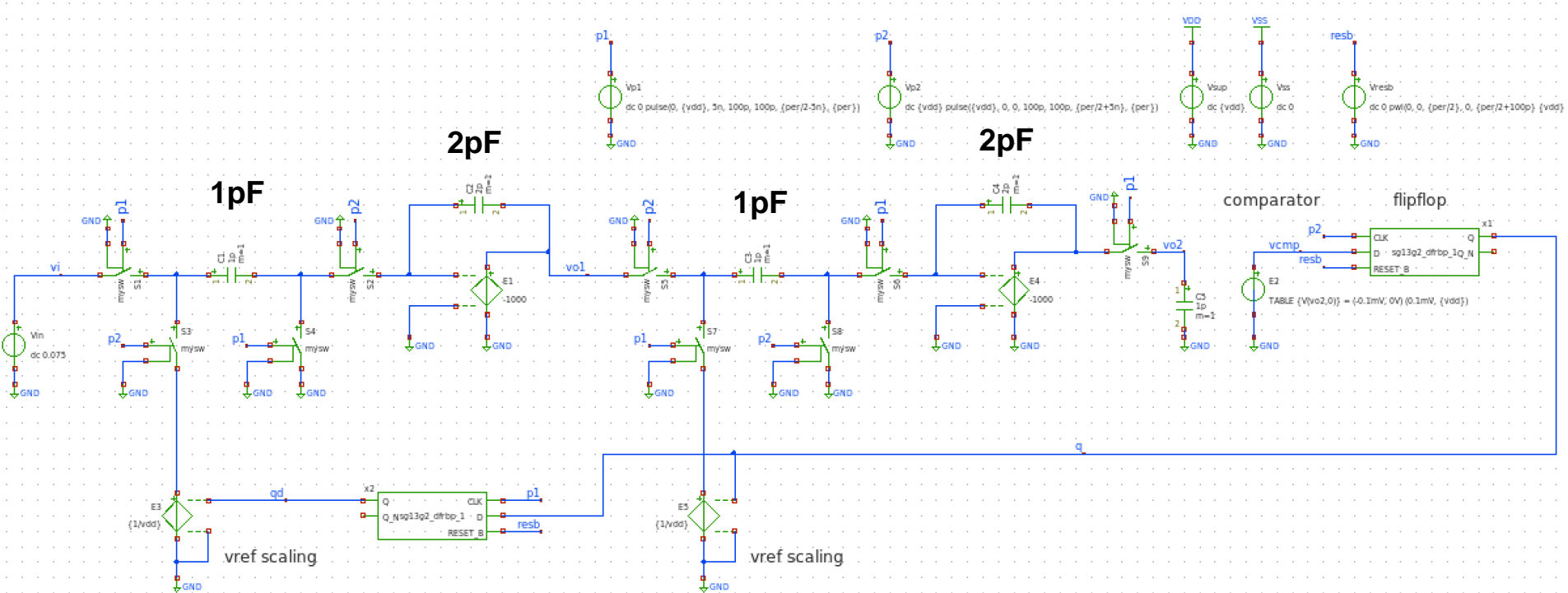


Looks a little complicated; better to stick integrators into a subcircuit + symbol

Simulation Result

 

Simulink

 


Close, but not the expected trajectory for int2 output. Why?

Postprocessing

```
# sample q and count number of ones
t = df['time']
ts = np.arange(1.5e-6, 1.5e-6+64*1e-6, 1e-6)
q = df['q']
interp_func = interp1d(t, q)
qsamp = interp_func(ts)
qsamp[qsamp > 0.5] = 1
qsamp[qsamp < 0.5] = 0
csum = np.cumsum(qsamp)
dout = np.cumsum(csum)
vin = 0.075*64.0*65.0/2.0
```
 
```
plt.figure(2)
plt.clf()
plt.plot(ts, dout, label="dout")
plt.plot([0, 65e-6], [vin, vin], label="vin")
plt.xlabel("time")
plt.legend(loc="lower right")
plt.grid()
plt.show()
```



```
dout[-1]
```

155.0


```
vin
```

156.0


Off by one quantization step after (64+1 us). Need one more clock cycle because of initial reset phase.

Probably OK, but best to do an input sweep to assess quantization error bounds (like we did in Simulink)


Voltage Range Considerations

 


Modified Schematic

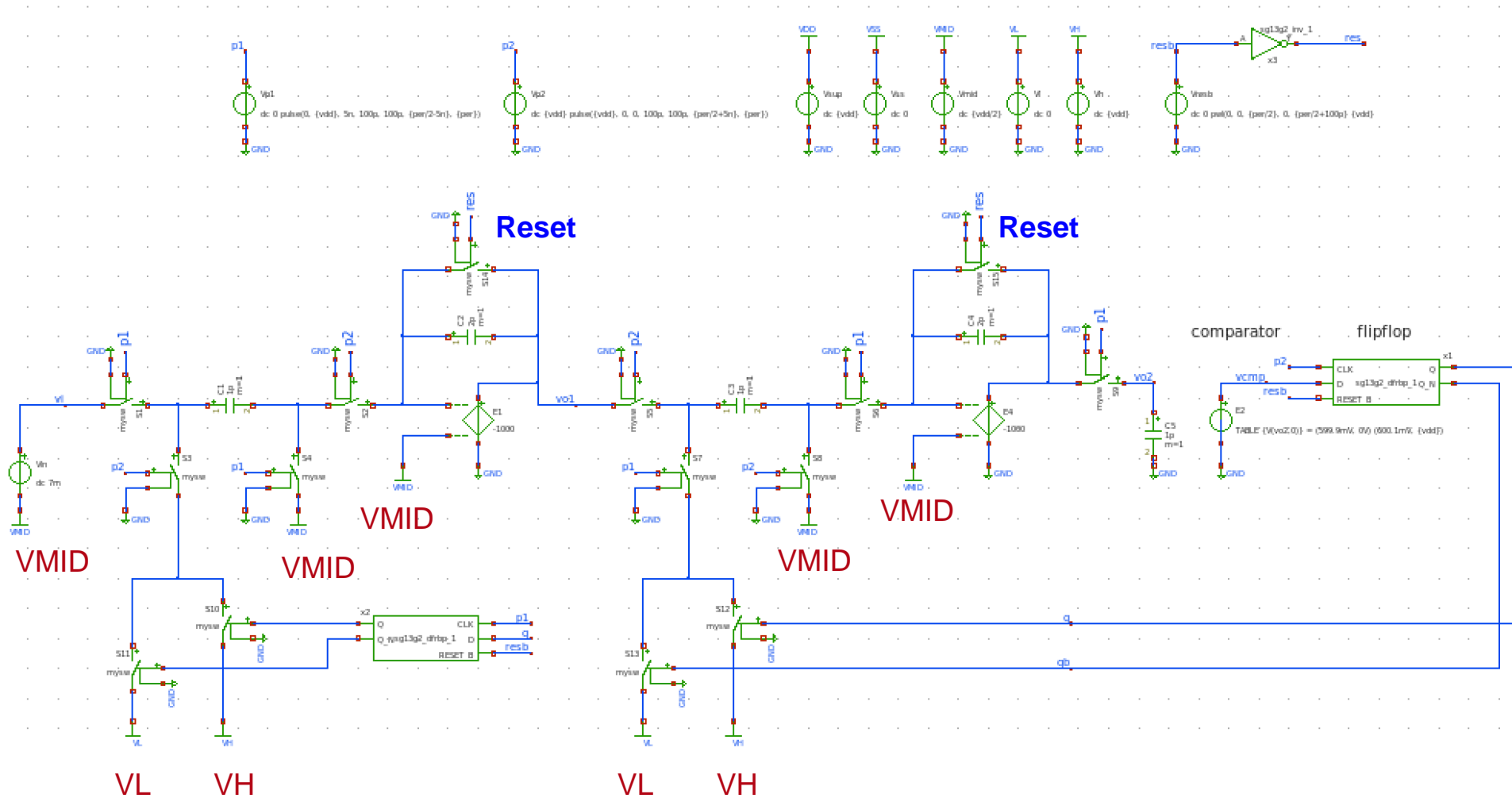

 $V_L = 0\text{ V}$, $V_H = V_{DD}$, $V_{in} = 7\text{ mV}$



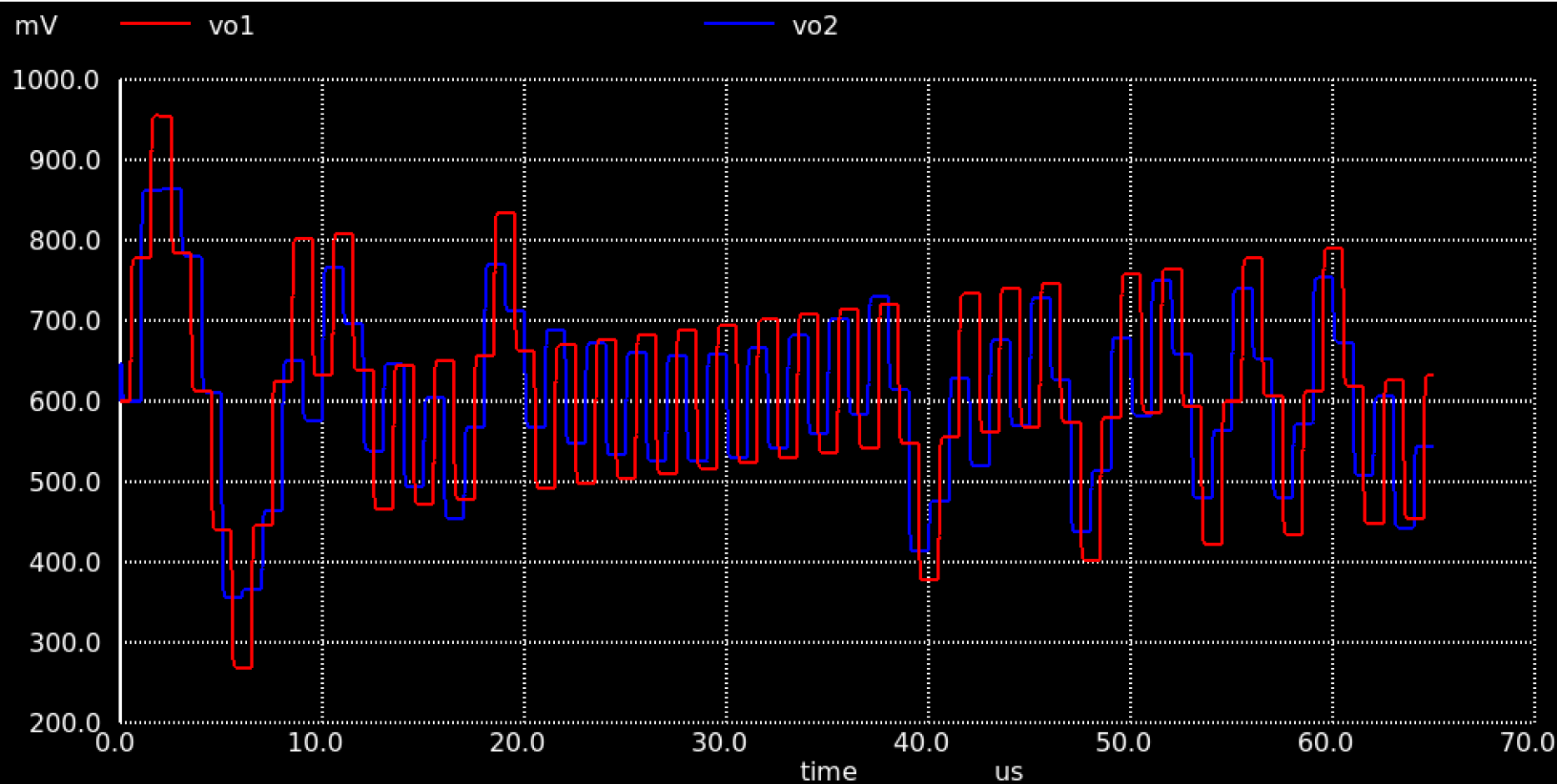$V_L = 0.25V$, $V_H = V_{DD} - 0.25V$, $V_{in} = 7\text{ mV}$



Looks good!

Simulation Settings

- You may have already noticed that these idealized circuit simulations are relatively slow
- This is partly because the circuits contains very fast transients, high-gain elements, sharp nonlinearities, huge impedance changes (R_{on}/R_{off})
- You may sometimes see convergence issues that can often be resolved making things slightly less ideal (e.g., $r_{off} = 10\text{gig} \rightarrow 1\text{ gig}$)

NGSPICE

```
.param temp=27 vdd=1.2 per=1u
.model mysw SW vt={vdd/2} ron=10k roff=1gig
.option method=gear reltol=1e-4

.control
save all
tran 1n 65u
plot vo1 vo2 q
set wr_singlescale
set wr_vecnames
wrdata tb_ideal_idsm2.txt vo1 vo2 q p1 p2
.endc
```

Next Steps

- Add second integrator (second-order modulator)
- Write some post-processing scripts
 - Detailed measurements
 - Emulate counters to create final digital output
- Increasingly “transistorize” the implementation
 - Shift voltages to practical levels (can’t have negative voltages)
 - Comparator
 - Inverter-based amplifier with CDS
 - MOSFET switches & clock generator