 


Amplifier

Boris Murmann

bmurmann@hawaii.edu



Technique Used in Our Template Design


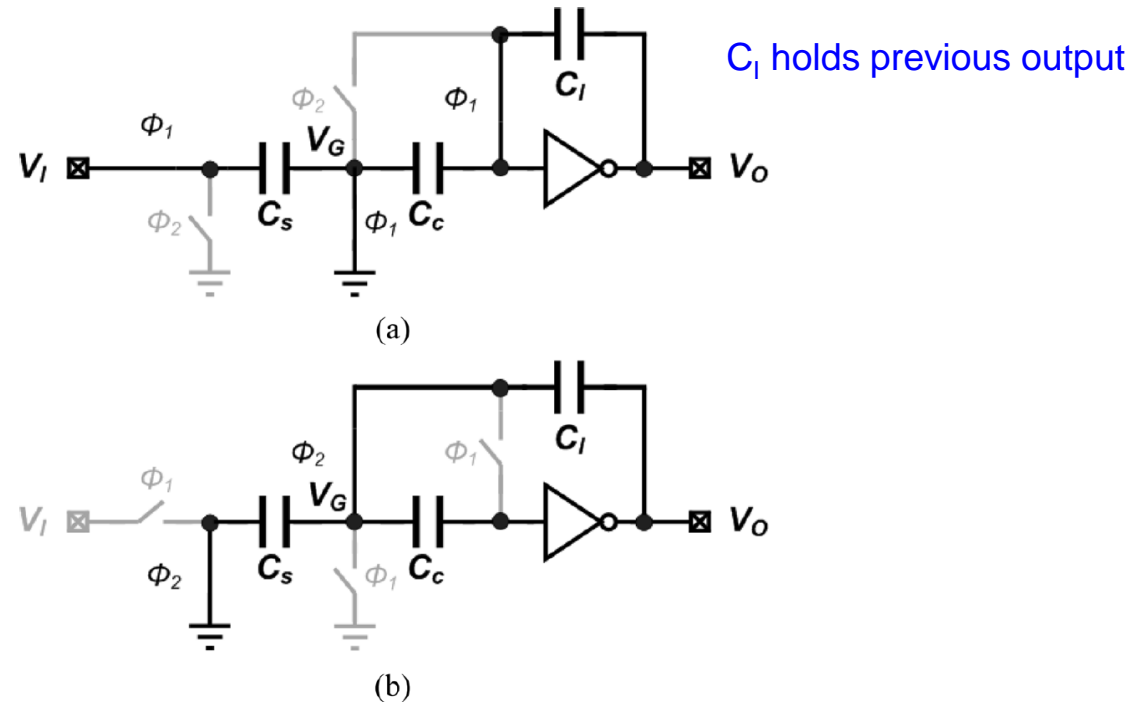
 


Fig. 4. Inverter-based SC integrator. (a) Sampling phase. (b) Integration phase.

Note: This approach addresses both offset & finite gain

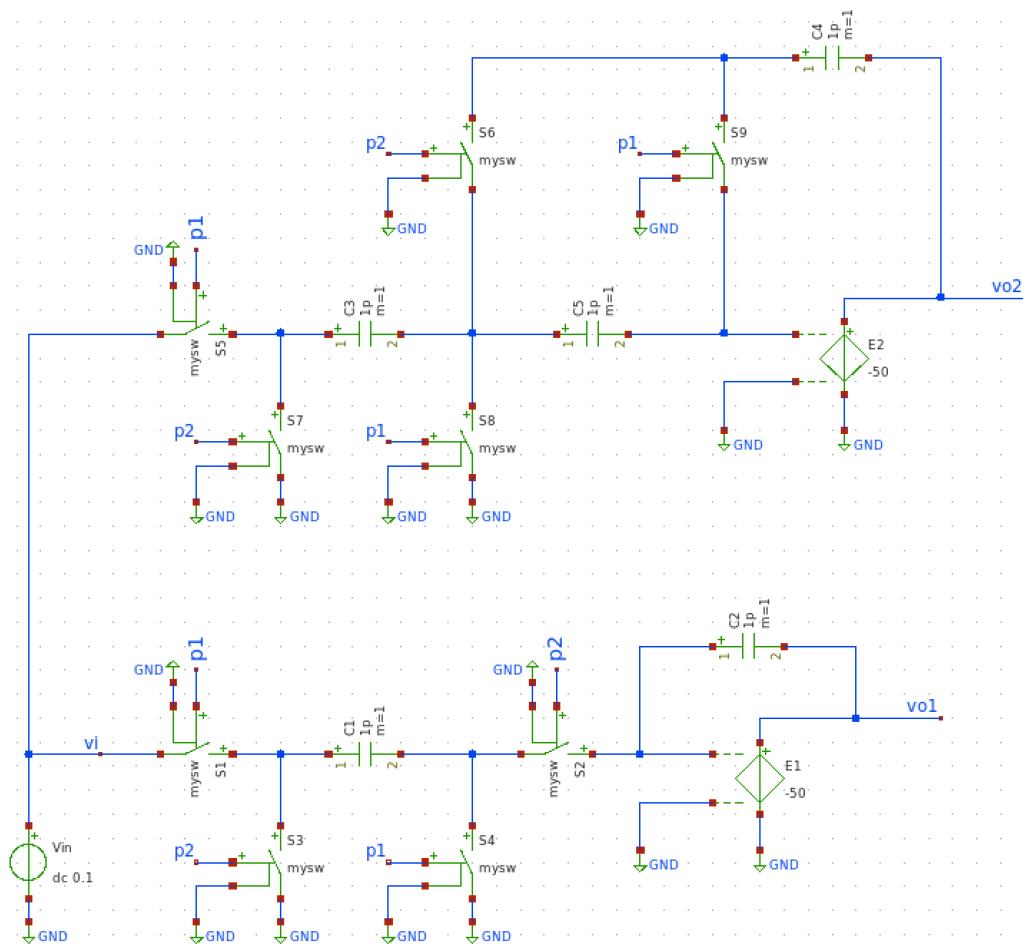Y. Chae et al., "A 2.1 M Pixels, 120 Frame/s CMOS Image Sensor With Column-Parallel ADC Architecture," in IEEE Journal of Solid-State Circuits, Jan. 2011. <https://ieeexplore.ieee.org/document/5641589>




NGSPICE

```
.param temp=27 vdd=1.2
.model mysw SW vt={vdd/2} ron=10k roff=10gig
.control
save all
tran 1n 50u
plot vo1 vo2
.endc
```

XSCHEM

Boris Murmann
/foss/designs/tb_chae_integ.sch

2024-02-07 17:32:24

 

Note: v_{o2} dips down a little during ϕ_1 during the finite gain; the ϕ_2 value is what matters


Numbers in Template Design

- Amplifier gain = 35 dB (56)
- Effective amplifier gain with enhancement = 50 dB (316)
- Improvement $\sim 5.6\times$

- Conversion rate = 440 kHz
- Clock rate = 48 MHz
- Oversampling ratio $M = 48 / 0.44 = 110$

- Effective gain is about 3x larger than oversampling ratio
 - I have mentioned 1x as a design boundary (q-noise explodes)

Inverter Gain in Our Technology

 

XSCHEM

Boris Murmann

/foss/designs/tb_inv_gain.sch

COMMANDS



```
.param temp=27
.param Wn=4u Wp={2*Wn} L=0.13u

.control
dc Vin 0.2 1 1m
alterparam L=1.5u
reset
dc Vin 0.2 1 1m
plot dc1.vout dc2.vout
plot deriv(dc1.vout) deriv(dc2.vout)
.endc
```

MODEL

```
.lib $::SG13G2_MODELS/cornerMOSlv.lib mos_tt
```

2024-02-07 21:43:41

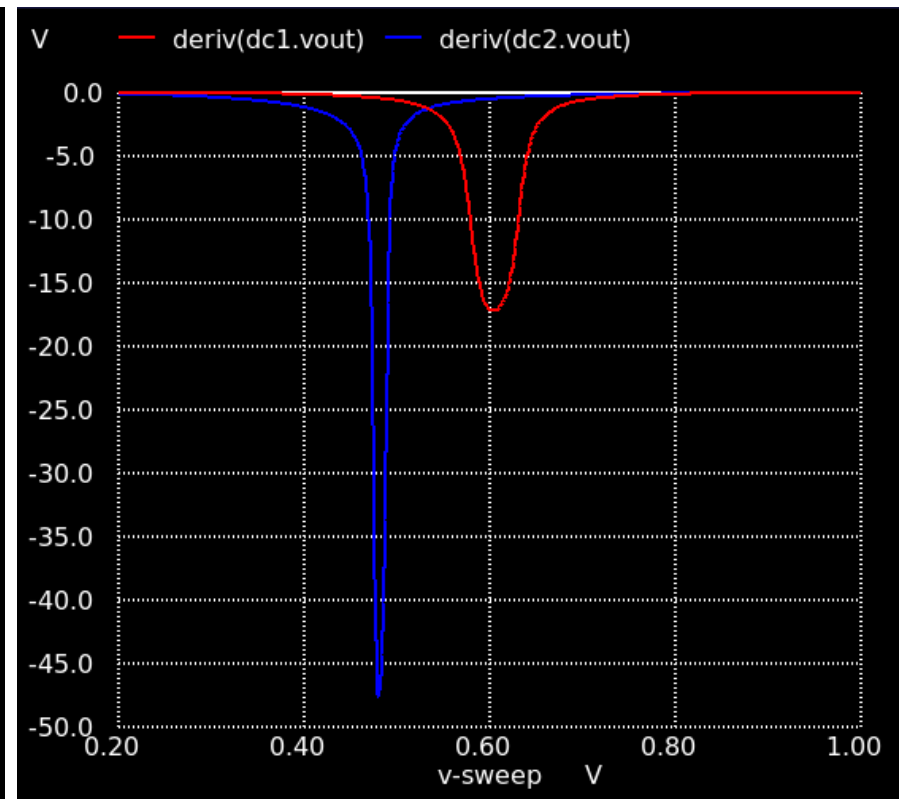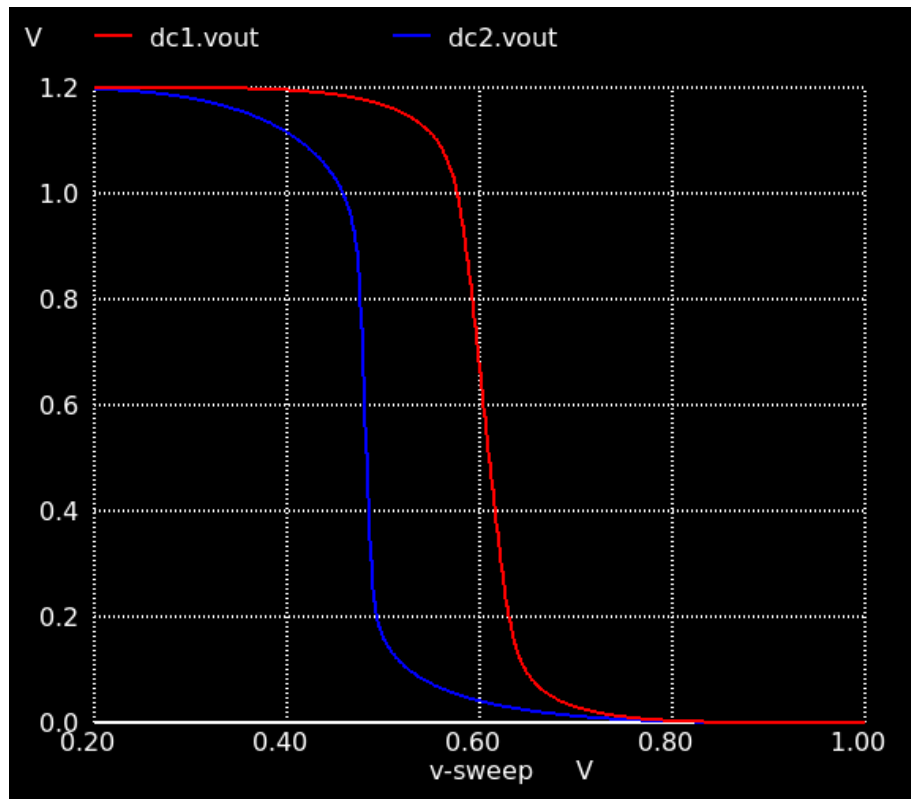

Next Steps

- Build integrator with inverter
 - Make sure circuit is practical (using VMID instead of GND, etc.)
 - Use reasonably large L for good initial gain
- Verify operation and see how much “effective gain” we can achieve
 - Compare response to idealized circuit without gain enhancement. Adjust VCVS gain until responses are equal → effective gain
 - Note that the improvement may be somewhat less than expected due to the inverter input capacitance
 - See Chae’s paper for details